

$$V_{in} \cdot \left(\frac{1}{r_{in}} + g_m + \frac{1}{r_o} \right) = i_{out}$$

Rout.

$$G_{m1} = -g_{m1} \quad \therefore A_{v1} = -g_{m1} (r_{o1} \parallel \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2})$$

$$\frac{V_{out}}{r_{\pi}} + g_m V_{in} = i_t$$

$$I_{D1} = I_{D2} \quad V_{OUT}$$

$$\frac{1}{2} \cdot 3.835 \times 10^{-5} \cdot \frac{100}{2.18-2.09} [(5-4)-0.8]^2 = \frac{1}{2} \cdot 1.342 \times 10^{-4} \cdot \frac{1}{5.16-2.09} \cdot (X-0.7)^2$$

$$x = \underline{2.39} = V_{OUT} \quad I_D = 3.835 \times 10^{-6}$$

$$V_{out}:$$

$$R_{out2} = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$g_{m2} = \frac{2 I_D}{V_{GS} - V_{TH}} = \frac{2 \cdot 3.835}{2.39 - 0.7} = 4.538$$

$$= \frac{1}{4.538} = \frac{1}{\text{gms}}$$

$$G_{m_1} = -g_{m_1}$$

$$R_{out1} = R_D \parallel r_o = R_{out2} \parallel r_{o1} = R_{out2}.$$

$$\therefore A_v = -g_{m1} \cdot R_{out2} = -\frac{g_{m1}}{g_{m2}}$$

$$g_{m1} = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2 \cdot 3.835}{5 - 4 - 0.8} = 38.35.$$

$$A_v = -8.45 \quad \therefore v_{out} = -8.45 \cdot 0.01 \sin \omega t.$$

$$= -0.0845 \sin \omega t, \quad \checkmark$$

(2) $I_{D1} + I_{D3} = I_{D2}$.

$$2 \cdot \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SQ} - V_{THP})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{THN})^2$$

$$V_{OUT} = 3.09 \quad I_{D1} = I_{D3} = 3.835 \times 10^{-5}, \quad I_{D2} = 7.67 \times 10^{-5}$$

for M_3 : $R_{out} = r_{o3} \cdot X$.

Then for M_1 : $G_{m1} = -g_{m1}$.

$$R_{out1} = R_D \parallel r_{o1} \Rightarrow$$

same as (1). $V_{out} = -8.45 \dots$

3. (A) for M_5 : $R_{out} = \frac{1}{g_{m5}} \parallel \frac{1}{g_{mb5}} \parallel r_{o5} = \frac{1}{g_{m5}} = R_D$.

for upper part: M_3 : $R_{out3} = r_{o3} \times$.

M_2 : $R_{out} = r_{o2} \times$.

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + r_{o2} \parallel (\frac{1}{g_{m2}} + g_{mb2})} = \frac{r_{o1}}{r_{o1} + \frac{1}{g_{m2}}} = -g_{m1}$$

$$R_{out} = (r_{o1} \parallel r_{o3}) \dots \parallel R_D = R_D = \frac{1}{g_{m5}}$$

$$\therefore A_v = \underline{-g_{m1} \cdot \frac{1}{g_{m5}}}$$

(B). ~~$A_{v1} = -g_m \cdot (R_D \parallel r_{o1}) = -g_{m1} (R_D \parallel r_{o1})$~~ \times

~~$A_{v2} = g_{m1} \cdot (r_{o1} \parallel \frac{1}{g_{m1}} \parallel R_D)$~~ \times

(C), for M_2 : $r_{o2} = R_{out1} = \infty$.

part A: $G_{m1} = g_{m1}$. $R_{out1} = r_{o1} \parallel R_S \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{mb1}}$
 $= \frac{1}{g_{m1}}$

$$A_{v1} = 1$$

second part: the same as (1)

third part: $G_m = -g_{m5}$.

$$R_{out} = R_D \parallel r_{o5} = R_D$$

$$\therefore \underline{A_{v3} = -g_{m5} \cdot R_D}$$

forth part: $A_v = 1$. $R_{out} = \frac{1}{g_{m6}}$ $G_m = g_{m6}$.



$$R_{out} = r_{o6} \parallel R_S \parallel \frac{1}{g_{m6}} \parallel \frac{1}{g_{mb6}}$$

$$\therefore A_v = \frac{1 - 1 - g_{m5} \cdot R_D \cdot 1 \cdot \frac{\frac{1}{g_{m6}}}{\frac{1}{g_{m6}} + R_L} V_{in}}{V_{in}}$$

$$= -g_{m5} \cdot R_D \cdot \frac{1}{1 + R_L \cdot g_{m6}}$$

4. A: NMOS

$$V_{AS} > V_{TH}. \quad V_x > 0.7,$$


$$\therefore V_x \in (0, 0.7) \quad I_x = 0.$$

$$V_{DS} < V_{AS} - V_{TH}.$$

$$\lambda < \lambda - 0.7 \quad \lambda. \quad \text{always sat:}$$

$$\therefore I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{AS} - V_{TH})^2 (1 + \lambda V_{DS}).$$
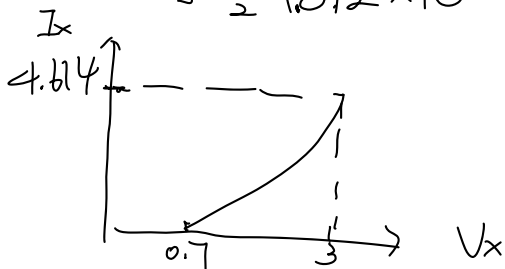
$$= \frac{1}{2} \cdot 1.342 \times 10^{-4} \cdot \frac{20}{2} \cdot (\lambda - 0.7)^2 (1 + 0.1 \lambda).$$



B: NMOS.

$$V_{AS} > V_{TH}. \quad \text{always } \sim$$

$$V_{DS} < V_{AS} - V_{TH}.$$

$$\lambda < 1 - 0.7.$$

$$\lambda \in (0, 0.3).$$

$$\lambda \in [0.3, 0.3]$$

$$V_{DS} > \dots$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{AS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$= \frac{1}{2} \cdot 1.342 \times 10^{-4} \cdot \frac{20}{2} \cdot (1 - 0.7)^2 (1 + \lambda \lambda)$$

$$= 6.22 \times 10^{-5} \sim 7.85 \times 10^{-5}$$

$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{AS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$= 1.342 \times 10^{-4} \cdot \frac{20}{2} \left[(1 - 0.7) \lambda - \frac{1}{2} \lambda^2 \right]$$

$$= 6.639 \times 10^{-5}$$





Upper = r_{o1} .


$$R_D = R + r_{o1}$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}}$$

$$V_{out1} = -g_{m3} (r_{o3} \parallel (R + r_{o1})) \frac{V_d}{a}$$

$$\therefore A_{DM} = -g_{m3} (r_{o3} \parallel (R + r_{o1}))$$



3(b) $A_v = \frac{V_{out1}}{V_{in}}$

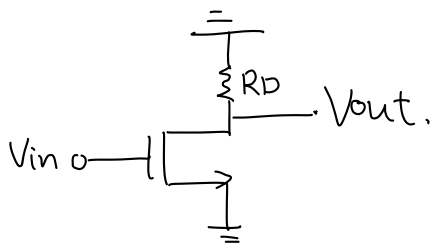

$$G_m = -g_{m1}$$



$$R_{out} = R_D \parallel r_{o1}$$
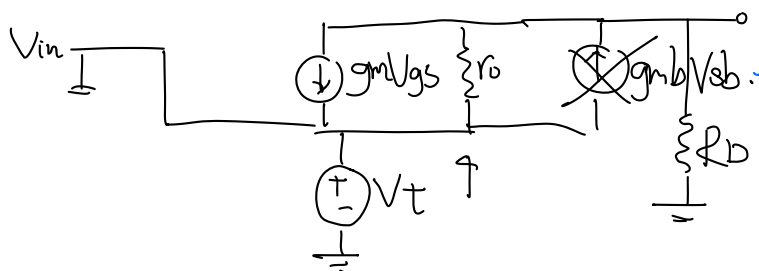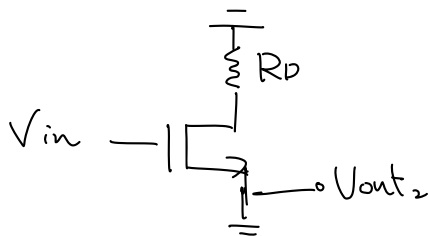
$$\therefore A_v = -g_{m1} (R_D \parallel r_{o1})$$



$$G_{m1} = \frac{i_{out}}{V_{in}} = -g_{m1}$$

$$R_{out} = \frac{V_t}{i_t} = \dots$$

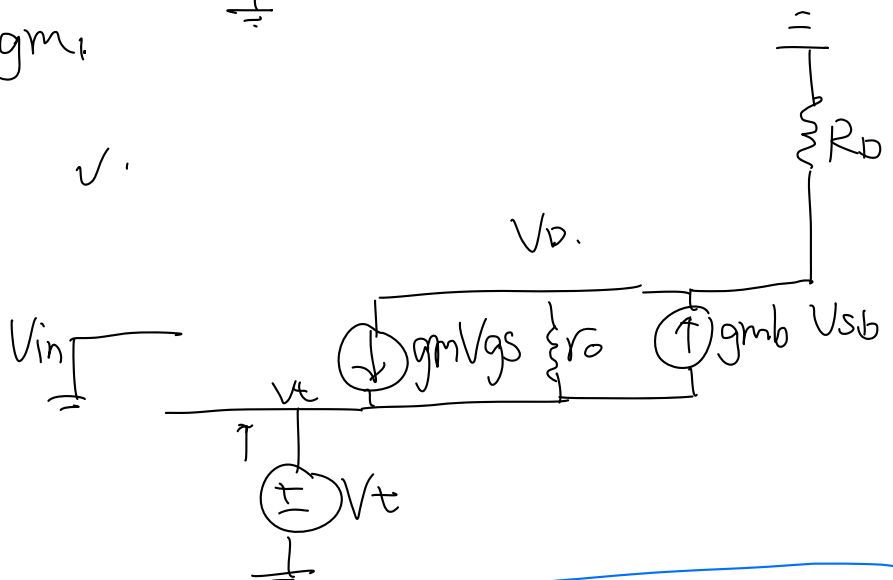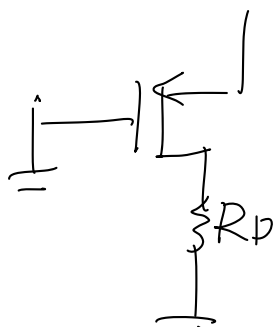

$$\frac{V_t}{i_t}$$

$$\begin{cases} i_t = g_m(-V_t) + \frac{V_D - V_t}{r_o} + (g_{mb}V_t) \\ g_m(-V_t) + \frac{V_D - V_t}{r_o} + \frac{V_D}{R_D} = g_{mb}V_t \end{cases}$$

$$\frac{V_D}{r_o} + \frac{V_D}{R_D} = g_m V_t + g_{mb} V_t + \frac{V_t}{r_o}$$

$$V_D = i_t \cdot R_D$$

$$i_t = g_m(-V_t) + \frac{i_t \cdot R_D - V_t}{r_o} + (-g_{mb}V_t)$$

$$g_m V_t + \frac{V_t}{r_o} + g_{mb} \cdot V_t = i_t \left(\frac{R_D}{r_o} - 1 \right)$$



$$R_{out} = \frac{V_t}{i_t} = \frac{\frac{R_D}{r_o} - 1}{g_m + \frac{1}{r_o} + g_{mb}}$$

$$= \frac{R_D - r_o}{g_m r_o + 1 + g_{mb} r_o}$$


$$R_{out} = R_D \parallel r_o$$

b

$$G_m = -g_m$$

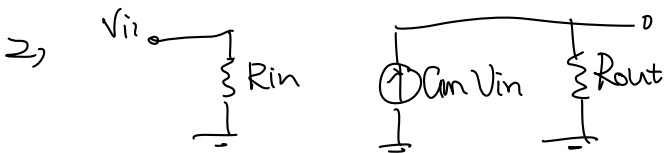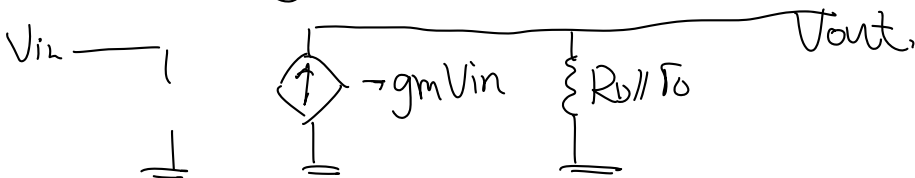

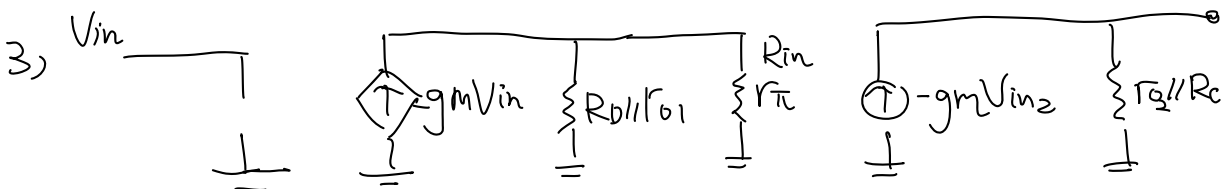
$$R_m = r_{\pi} \quad G_m = -g_m \quad R_{out} = r_o \parallel R_c$$



$$A_{v1} = -g_{m1} (R_D \parallel r_{o1})$$

$$R_{out1} = R_D \parallel r_{o1}$$

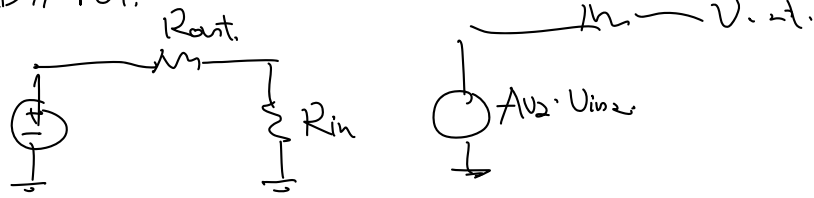

$$\underline{A_{v1} \cdot V_{in} \cdot \frac{R_{in}}{R_{out1} + R_{in}} \cdot A_{v2}} = \underline{V_{out}}$$

$$\frac{R_{out1} R_{in2}}{R_{out1} + R_{in2}} \cdot R_{out2}$$

S3/2.


R_{out}

$$R_{oT} = r_{o3}$$

$$R_{out} = (g_{m2} + g_{mb2}) r_{o2} r_{o3} + r_{o2} + r_{o3}$$

$$R_{E2} = r_{o1}$$
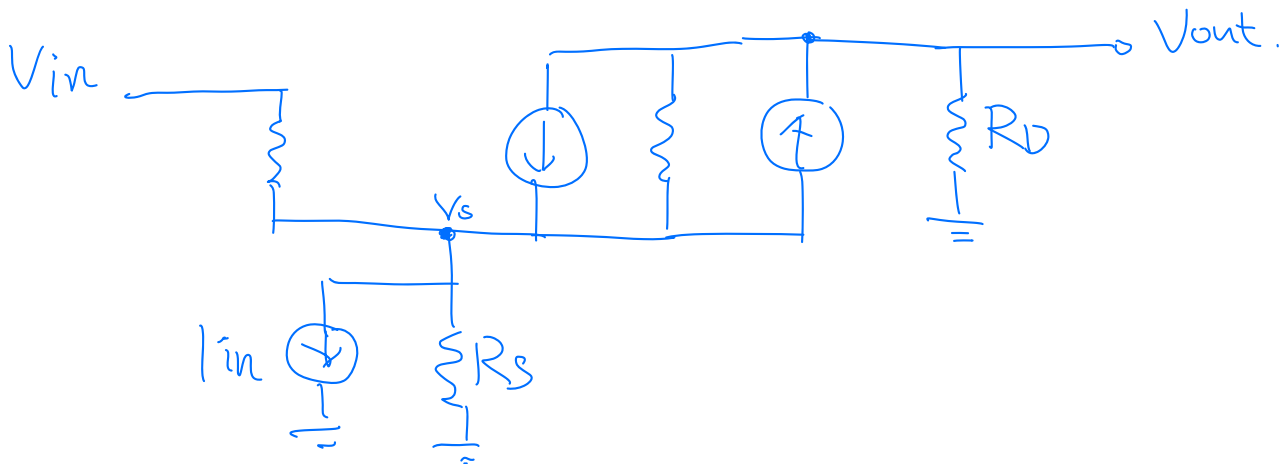
$$[(r_{o1} \parallel R_2) + R_1] \parallel [(g_{m2} + g_{mb2}) r_{o2} r_{o3} + r_{o2} + r_{o3}] \parallel R_D$$



$$\begin{cases} \frac{V_{out}}{R_D} - g_{mb2}(V_s - V_{out}) + \frac{V_{out} - V_s}{r_{o3}} + g_{m2}(V_{out} - V_s) = 0 \\ g_{mb1}(V_s - V_{out}) - g_{m1}(V_{out} - V_s) + \frac{V_s - V_{out}}{r_{o1}} + \underline{I_{in} + \frac{V_s}{R_s}} = 0 \end{cases}$$

$$I = \frac{V_{DD} - V_{OUT}}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{THN})^2 (1 + V_{DS})$$

$$= \frac{V_s}{R_s} + I_{in}$$

$$\sqrt{\frac{\mu_n \frac{X}{2-2 \cdot 0.8}}{\mu_p \frac{5}{2-2 \cdot 0.9}}} = -6.$$

$$X = 51.99.$$

$$P: V_{SD} > V_{SA} - |V_{THP}|$$

$$N: V_{DS} > V_{AS} - V_{TH}$$

$$5 - V_{OUT} \Rightarrow V_{DD} - V_{OV} = \dots \checkmark.$$

$$V_{OUT} > V_{in} - V_{TH}$$

$$I_D = I_b$$

$$\cancel{\frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}}} \cdot (V_{AS} - V_{TH})^2 = \cancel{\frac{1}{2} \mu_p C_{ox} \frac{W}{L_{eff}}} (V_{SA} - V_{TH})^2$$

$$350 \cdot (V_{in} - 0.7)^2 \cdot \frac{52}{2-2 \cdot 0.8} = 100 \cdot \frac{5}{2-2 \cdot 0.9} \cdot (5 - V_{OUT} - 0.8)^2$$