



JOINT INSTITUTE


交大密西根学院

BJT and BJT Circuit

Ve311 Electronic Circuits (Summer 2020)


Dr. Chang-Ching Tu

For a general amplifier model:

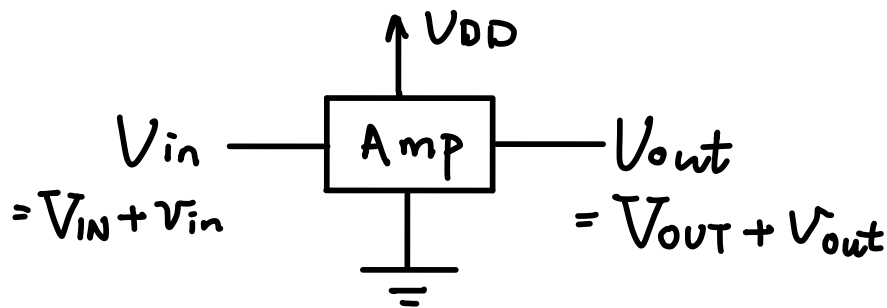

$$V_{out} = \underbrace{V_{OUT}}_{\text{DC complete circuit}} + A_v \cdot v_{in}$$

DC sweep:

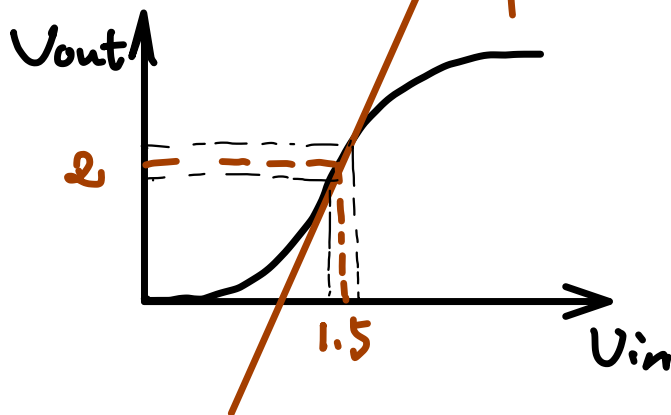


Slope = 10 Suppose $V_{in} = 1.5 + 0.001 \sin(2\pi 60t)$
 $V_{out} = 2 + 0.01 \sin(2\pi 60t)$


$$A_v = \left. \frac{dV_{out}}{dV_{in}} \right|_{@V_{in}} = \frac{\overbrace{v_{out}}^{V_{out}}}{\overbrace{v_{in}}^{V_{in}}} = 10$$

final 重要

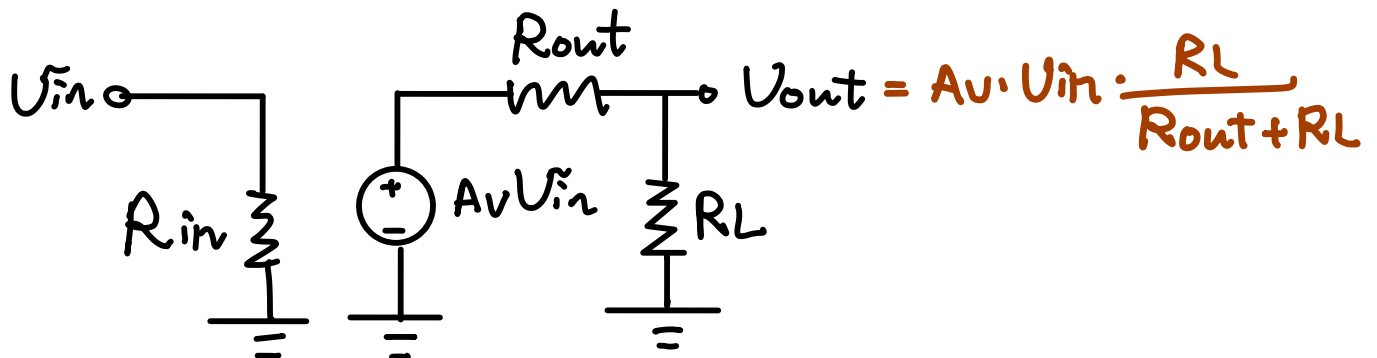Generalized small-signal model: (more important in final exam, no need to understand this deeply for now)



Summary

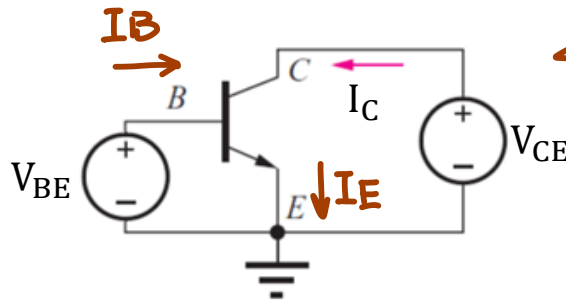

$$V_{CE} \geq V_{BE}$$

\Rightarrow Forward - Active

Ideal case

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$\alpha = \frac{I_C}{I_E} \cong 1$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$$V_A = \infty$$



$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} = 1$$

$$\beta = \frac{I_C}{I_B} = \infty$$

$$I_E = I_B + I_C$$

I_S is a constant in the spice model.

$$I_C = I_E$$

完全理想：门电压 V_{BE} 一定， $I_C = I_E$ 固定

第一种非理想：门漏电 $I_E = I_B + I_C$.

第二种非理想：随着 $V_{CE} \uparrow$, $I_C \uparrow \Rightarrow$ Early effect $V_A \neq \infty$.



集电压对集电流有影响

I_C vs V_{CE} and I_C vs V_{BE}
in Forward-Active Region

I_C vs V_{CE} (not considering Early Effect)


7

At given V_{BE} , DC sweep V_{CE}

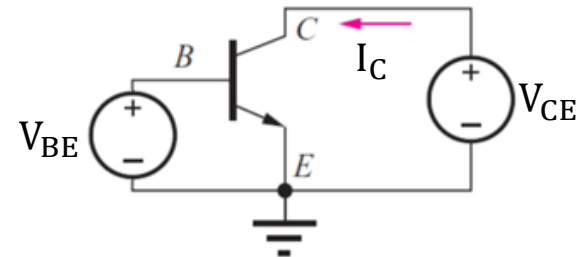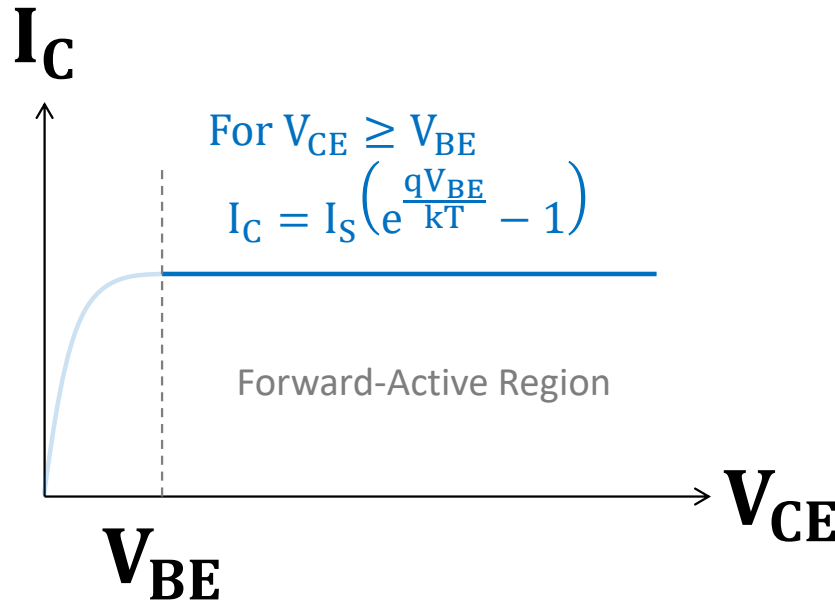


I_C vs V_{CE} (considering Early Effect)

At given V_{BE} , DC sweep V_{CE}

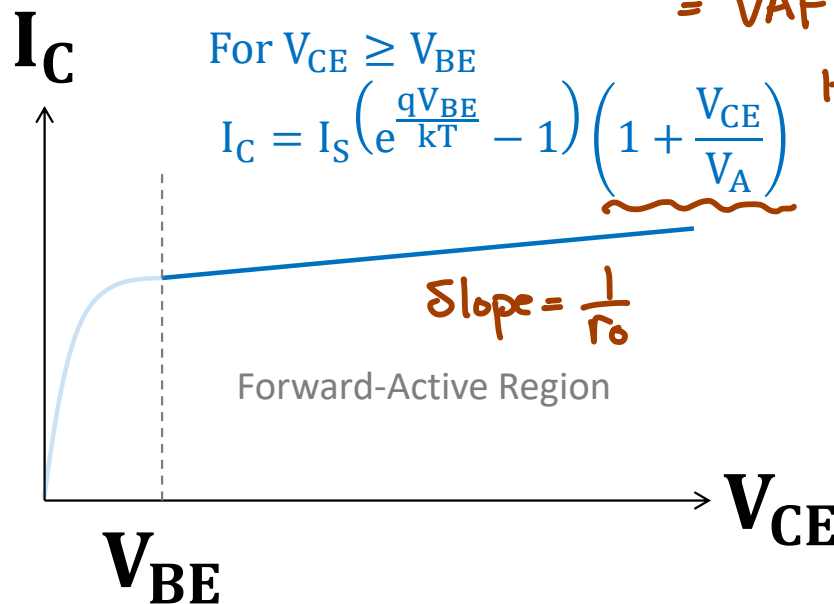

V_A is a constant
= VAF in Pspice model

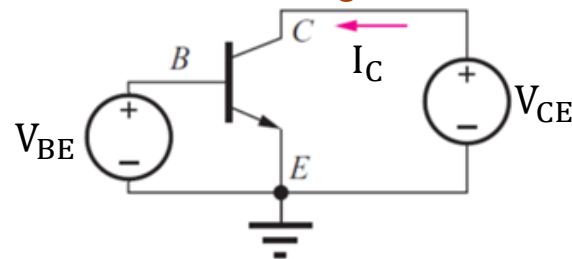
If $V_A \rightarrow \infty$,
no early-effect



V_A is a constant in the spice model.

I_C vs V_{BE}


At given V_{CE} , DC sweep V_{BE}

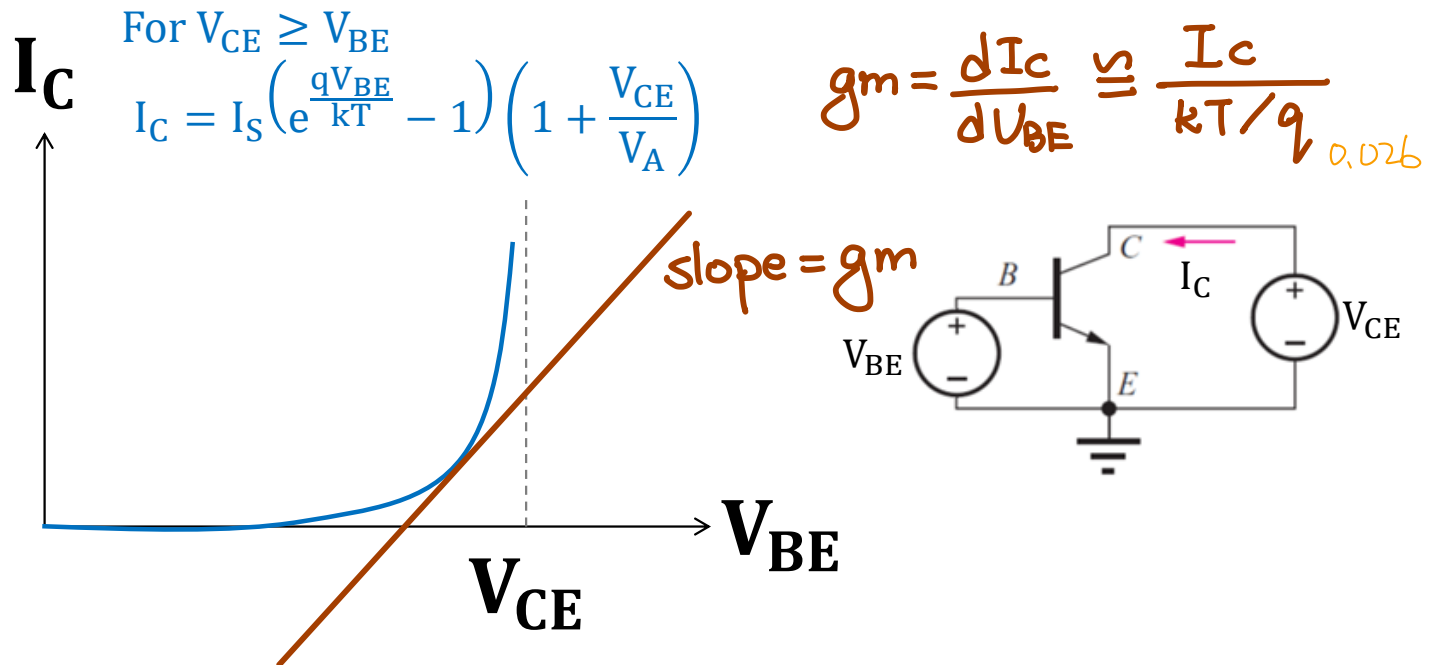


Small-Signal Model

Conclusion first:


For a BJT as:

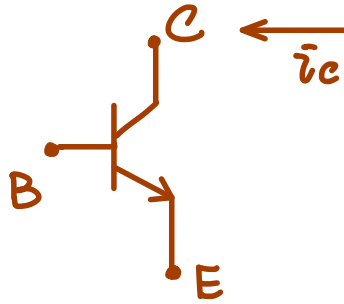

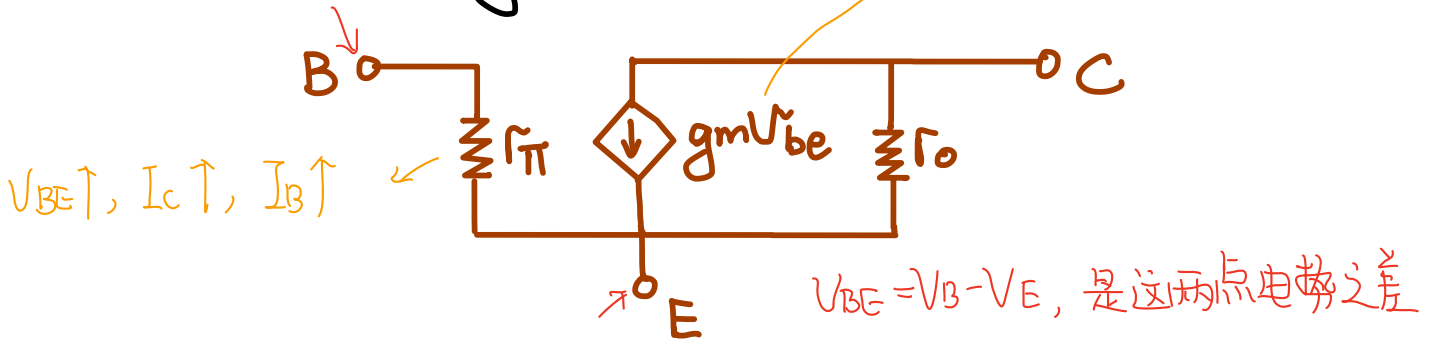
Its small signal model is: $I_c = I_s (e^{\frac{V_{be}}{kT/q}} - 1)$...



Typical circuit:

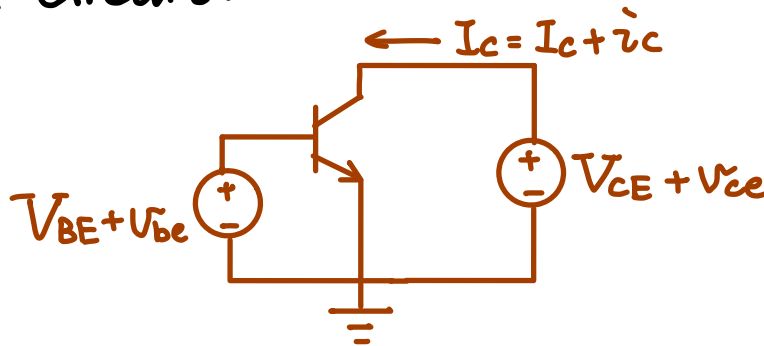

Small signal model:

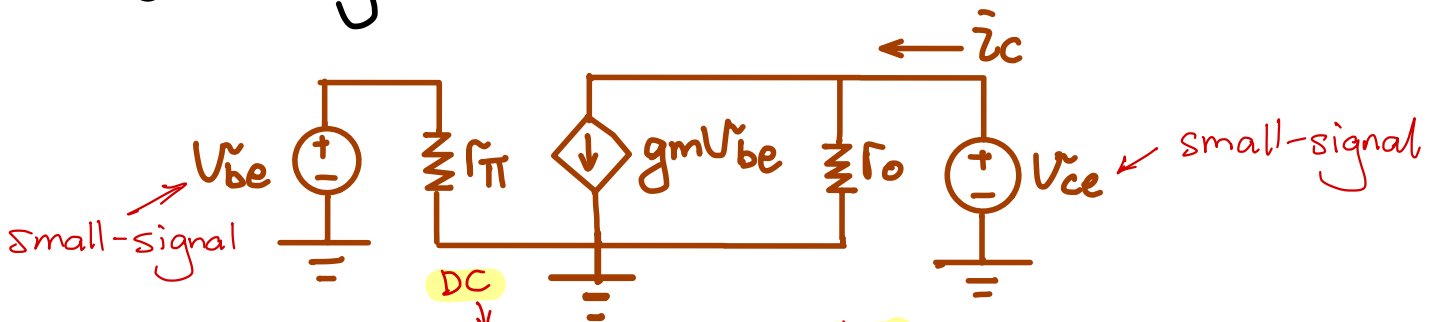

用DC求

$$I_c = I_s (e^{\frac{qV_{BE}}{kT}} - 1) (1 + \frac{V_{CE}}{V_A})$$

$$g_m \approx \frac{I_c}{kT/q}$$


$$r_o \approx \frac{V_A}{I_c} \leftarrow V_{AF} \text{ in Pspice model}$$

$$r_{\pi} = \frac{\beta}{g_m} \leftarrow \text{BF in Pspice model}$$

If no early-effect.
 $V_A \rightarrow \infty, r_o \rightarrow \infty$

Hybrid- π Model (how to get g_m and r_π)

Complete circuit:

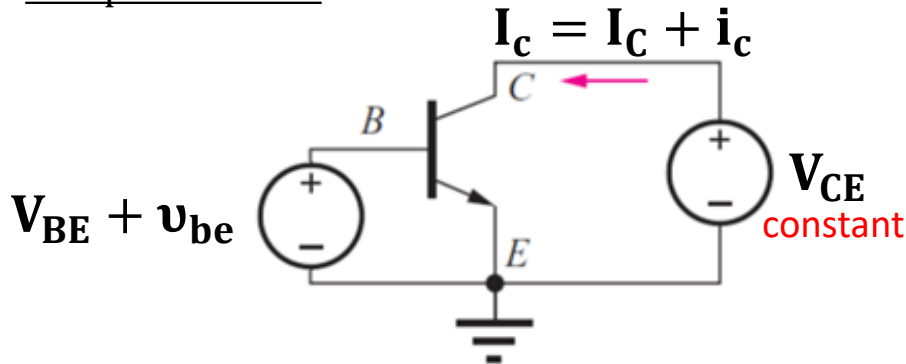


$$V_{CE} \geq V_{BE}$$

\Rightarrow Forward – Active

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Small-signal circuit:

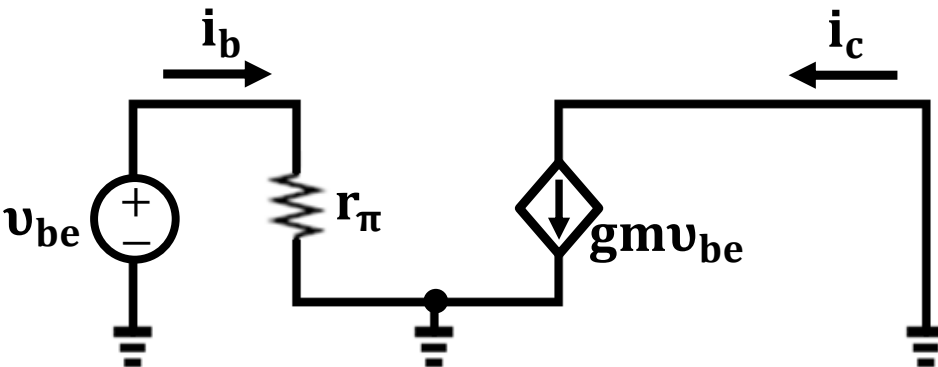


$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{gm}{\beta}} = \frac{\beta}{gm}$$

$$gm = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q}$$

Hybrid- π Model (how to get r_o)

Complete circuit:

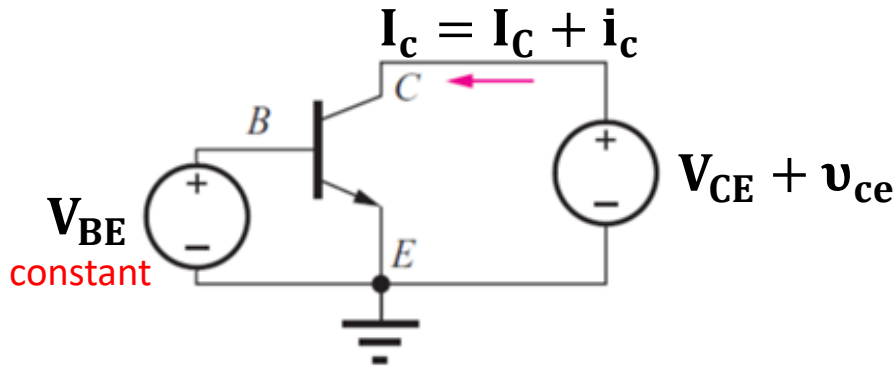


$$V_{CE} \geq V_{BE}$$

\Rightarrow Forward – Active

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Small-signal circuit:

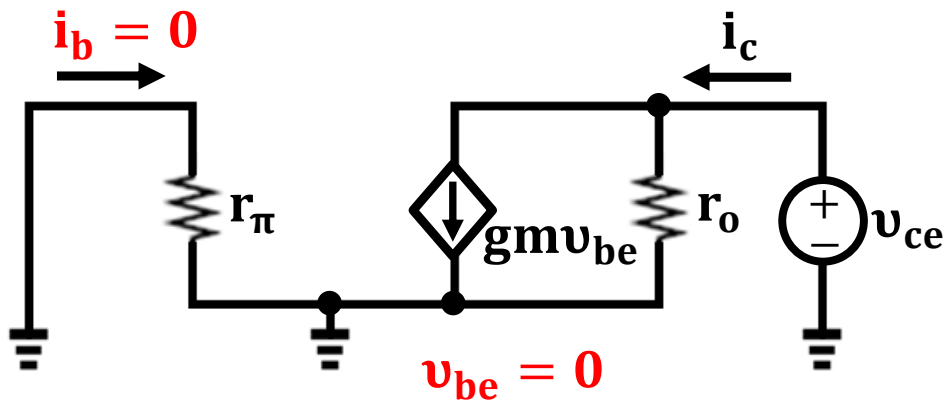


$$r_\pi = \frac{1}{\frac{dI_B}{dV_{BE}}} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{gm}{\beta}} = \frac{\beta}{gm}$$

$$gm = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q}$$



$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \cong \frac{V_A}{I_C}$$

Note: Why do we have r_o , r_{π} , g_m in small signal model?
(Skip this page if you already understand)

①

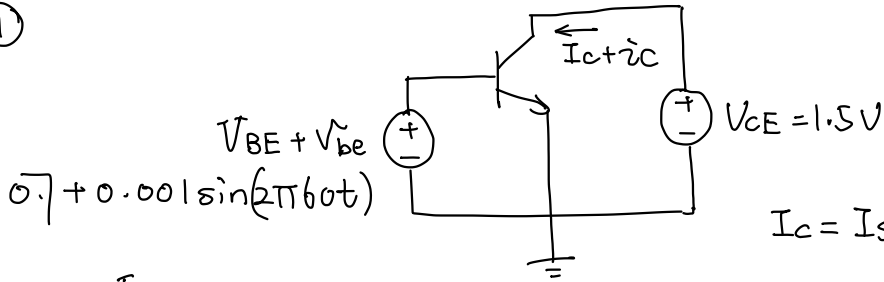
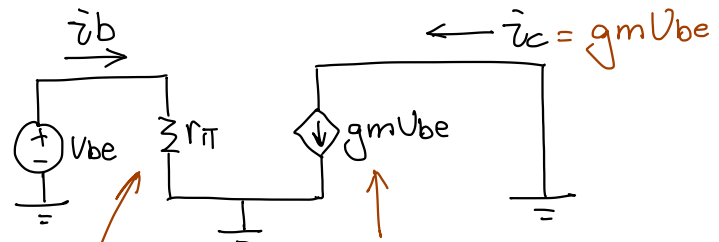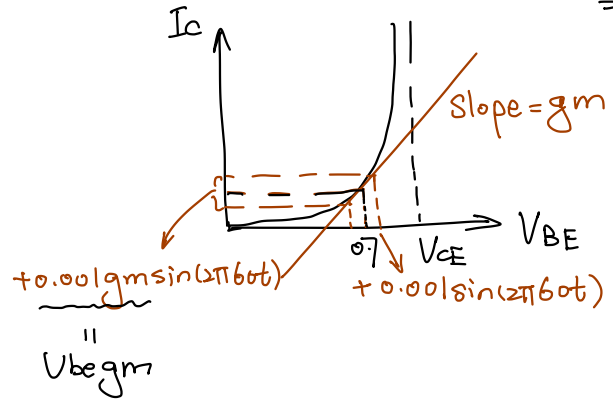
$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$






So, here's a dependent current source that simulates $i_c = g_m v_{be}$

Since $\beta = \frac{I_C}{I_B} = 100$

If $v_{be} \uparrow \Rightarrow i_c \uparrow \Rightarrow i_b \uparrow$

"feels like" r_{π} exists

② HF:

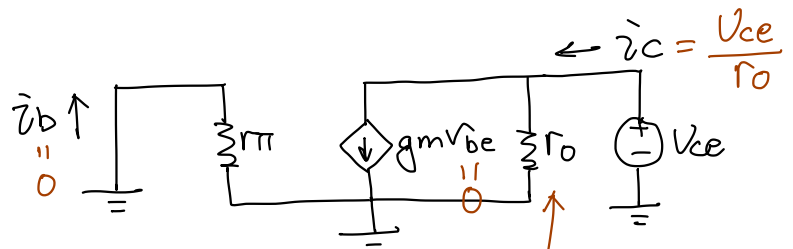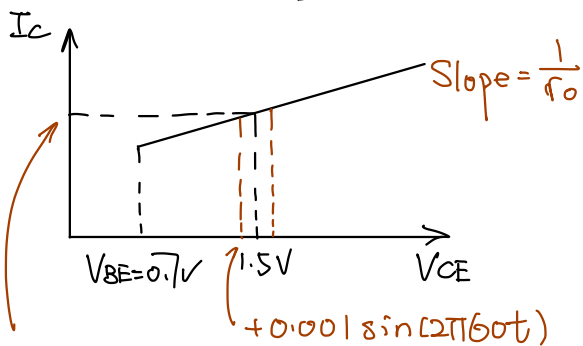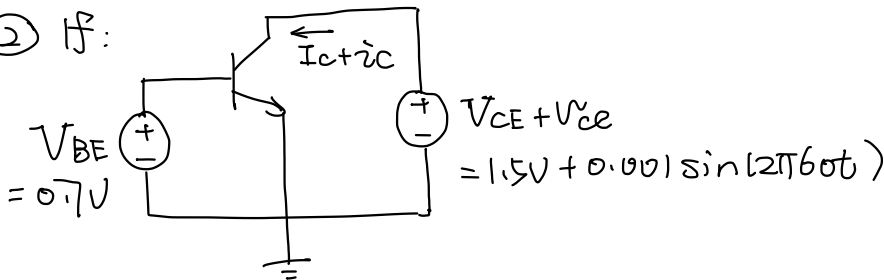

since $i_c = \frac{v_{ce}}{r_o}$


"feels like" r_o exists here

$\frac{+0.001}{r_o} \sin(2\pi 60t)$
 $\frac{v_{ce}}{r_o}$



Common-Emitter Amplifier

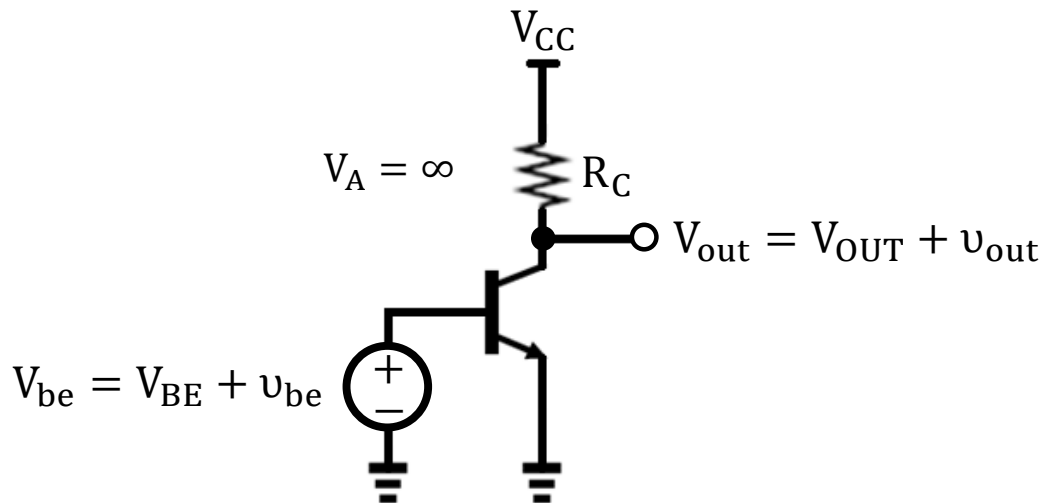Common-Emitter Amplifier ($V_A = \infty$)




• DC Analysis

$$V_{OUT} = V_{CC} - I_C R_C$$

$$= V_{CC} - \frac{A_q D_n n_i^2}{N_a W_B} \left(e^{\frac{q V_{BE}}{kT}} - 1 \right) R_C$$

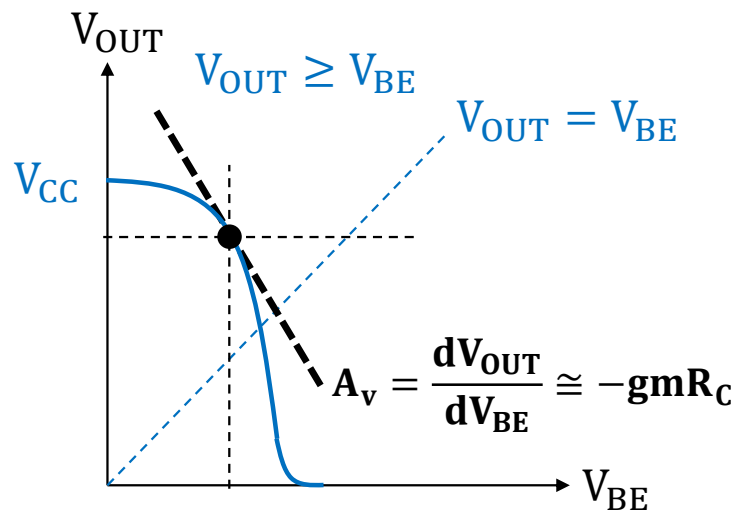
$$A_v = \frac{dV_{OUT}}{dV_{BE}} \cong -\frac{I_C}{kT/q} R_C = -gm R_C$$




Common-Emitter Amplifier ($V_A = \infty$)

$$A_v = \frac{dV_{out}}{dV_{BE}} = \boxed{\frac{v_{out}}{v_{be}}}$$

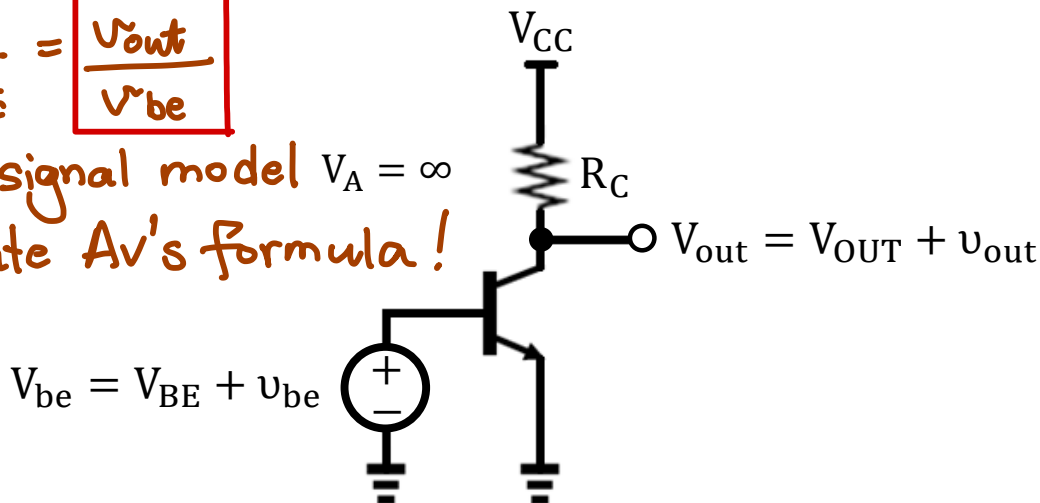Use small-signal model $V_A = \infty$
to calculate A_v 's formula!




• Small-Signal Analysis

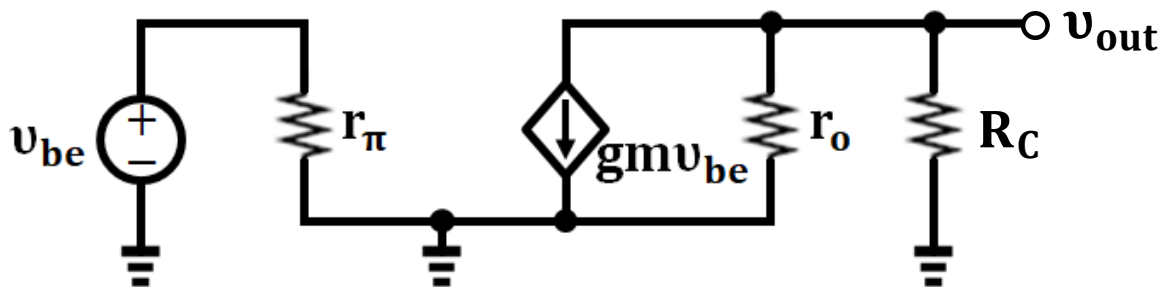

$$A_v = \frac{v_{out}}{v_{be}} = -gm(R_C \parallel r_o) = -gmR_C \quad (\text{since } r_o = \infty)$$

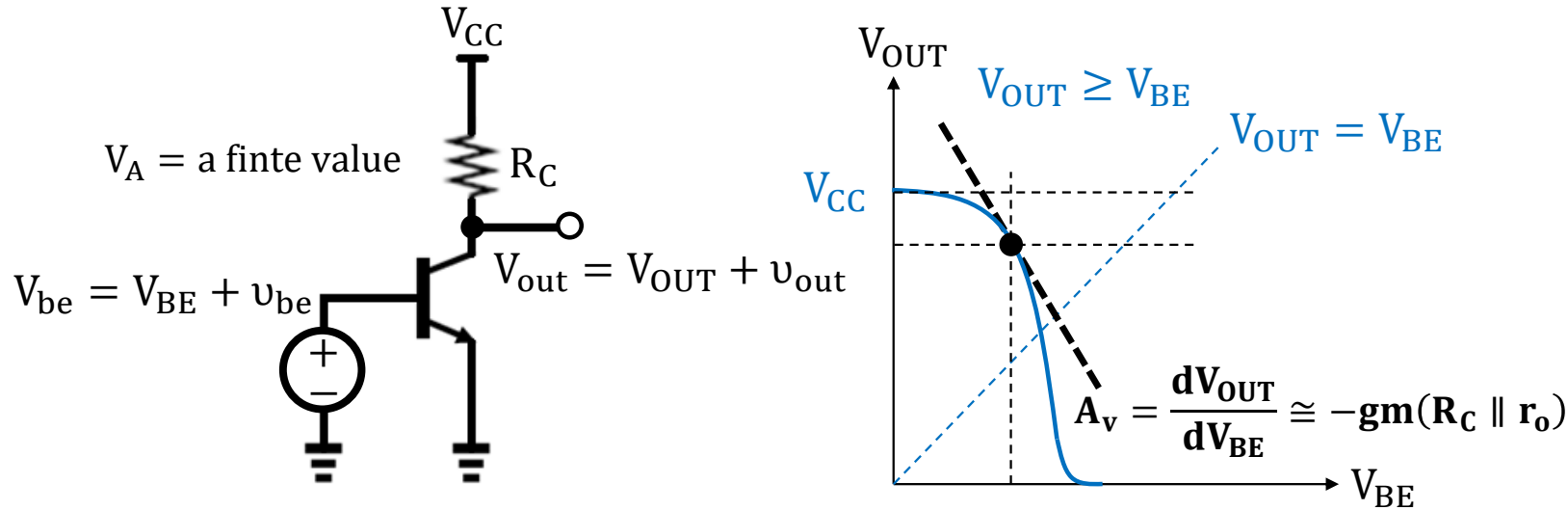Common-Emitter Amplifier ($V_A = \text{a finite value}$) ¹⁶




• DC Analysis

$$V_{OUT} = V_{CC} - I_C R_C = V_{CC} - I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{OUT}}{V_A} \right) R_C$$


$$\frac{dV_{OUT}}{dV_{BE}} = -\frac{q}{kT} I_S e^{\frac{qV_{BE}}{kT}} \left(1 + \frac{V_{OUT}}{V_A} \right) R_C - I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \frac{1}{V_A} \frac{dV_{OUT}}{dV_{BE}} R_C \cong -gm R_C - \frac{1}{r_o} \frac{dV_{OUT}}{dV_{BE}} R_C$$

$$A_v = \frac{dV_{OUT}}{dV_{BE}} \cong -gm(R_C \parallel r_o)$$

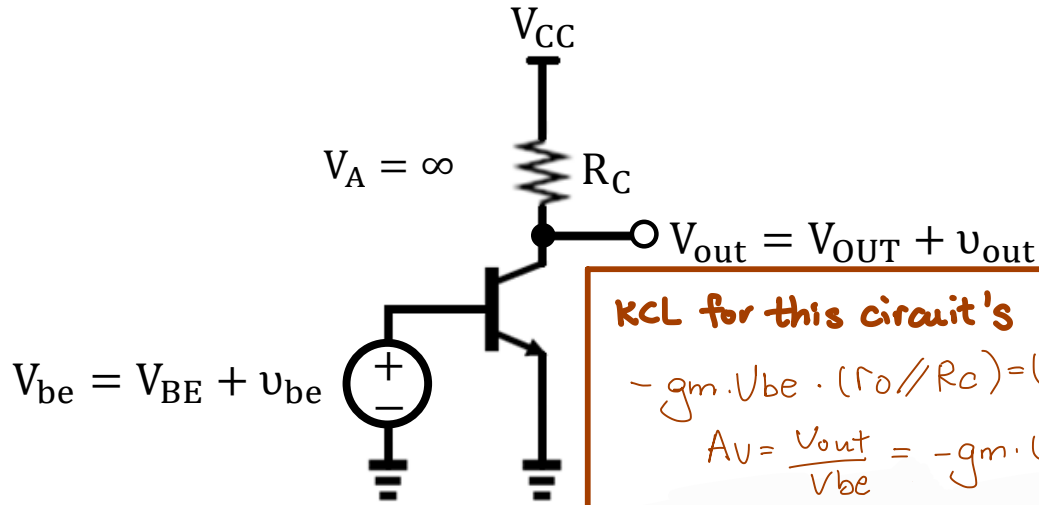Common-Emitter Amplifier ($V_A = \text{a finite value}$)¹⁷



- Small-Signal Analysis

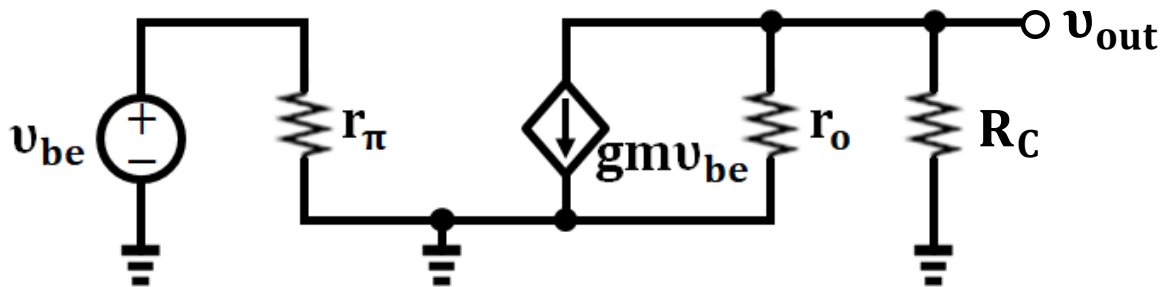

对不同 circuit 求 A_v 用
KCL 分析 small-signal
circuit

$$A_v = \frac{v_{out}}{v_{be}} = -g_m (R_C \parallel r_o)$$

Convert to small-signal model:

DC voltage \rightarrow short to small-signal ground


DC current \rightarrow open circuit

$R \rightarrow$ still R


capacitor \rightarrow short circuit

Ex:

✓ Complete circuit:

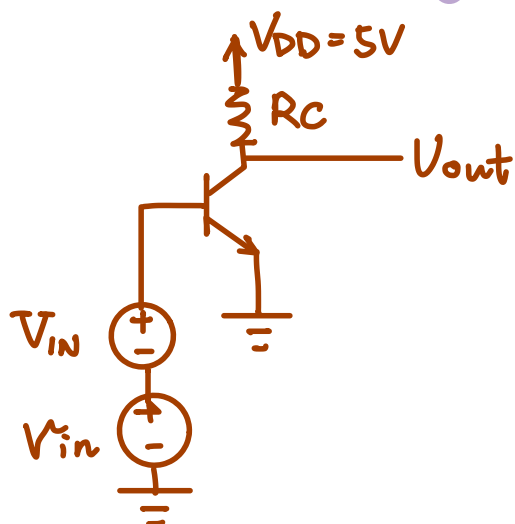


Small-signal:

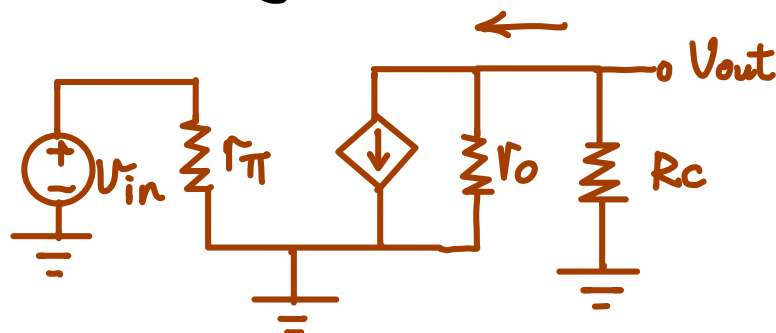


$$A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_C)$$

✓ Complete circuit:

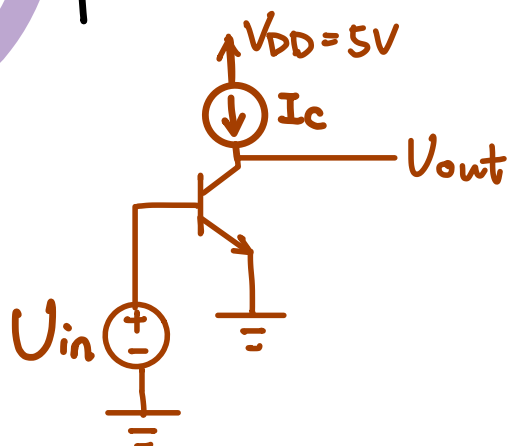


Small-signal:

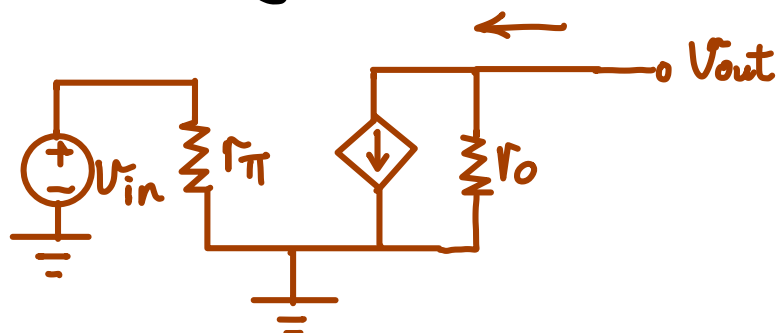


$$A_v = \frac{V_{out}}{V_{in}} = -g_m r_o$$

Complete circuit:

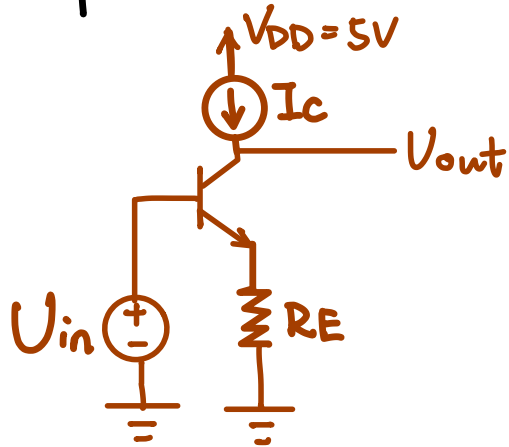

* Small-signal:

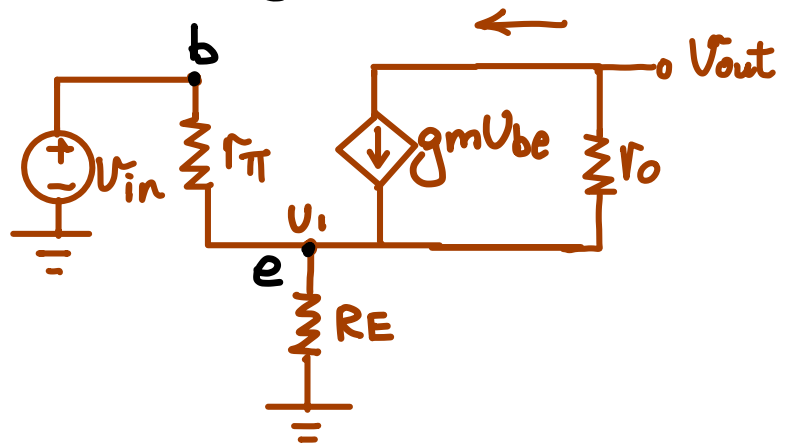


* mind U_{be} used in $g_m U_{be}$ doesn't necessarily equals to U_{in} !


$$\text{KCL: } \begin{cases} \frac{U_1}{R_E} = \frac{U_{in} - U_1}{r_{\pi}} + g_m U_{be} + \frac{U_{out} - U_1}{r_o} \\ U_{be} = U_{in} - U_1 \\ g_m U_{be} + \frac{U_{out} - U_1}{r_o} = 0 \end{cases}$$

\Rightarrow Calculate $A_v = \frac{U_{out}}{U_{in}}$

Complete circuit:

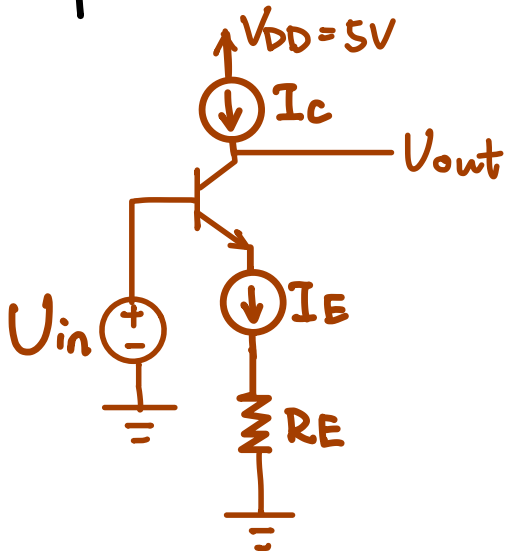


Small-signal:

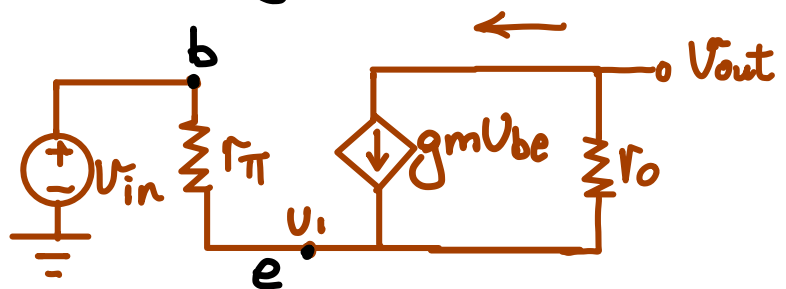


↑ open circuit here

$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_{in}}{V_{in}} = 1$$

✓ Complete circuit:

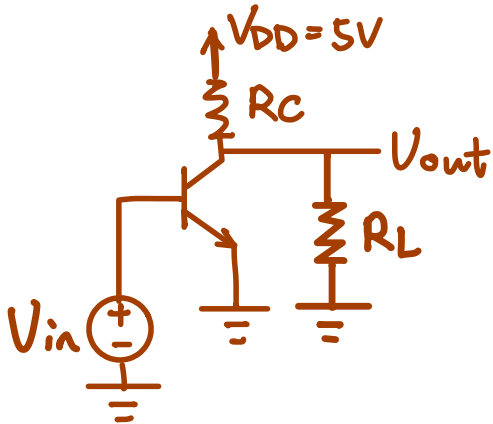


Small-signal:

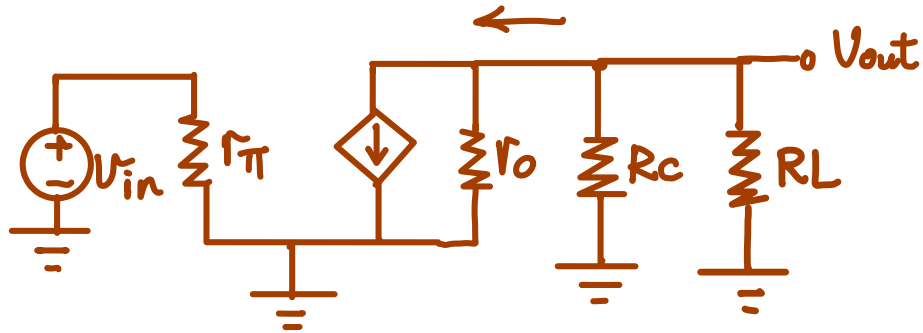


$$A_v = \frac{U_{out}}{U_{in}} = -g_m (r_o \parallel R_c \parallel R_L)$$

✓ Complete circuit:

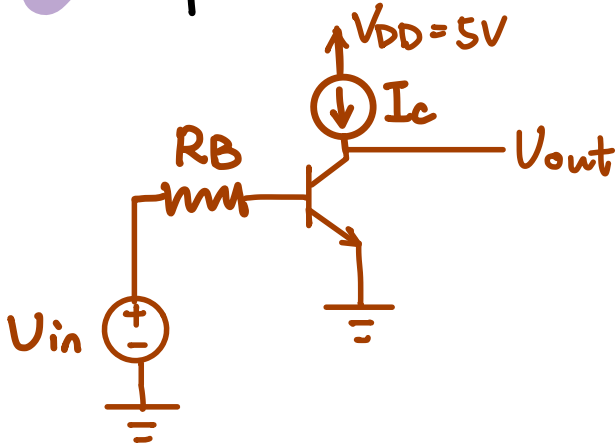


Small-signal:

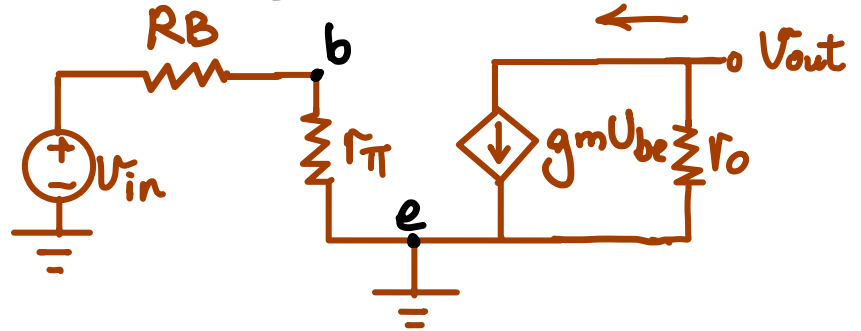


$$\text{KCL: } U_{be} = U_{in} \frac{r_\pi}{r_\pi + R_B}$$

$$A_v = -g_m r_o \cdot \frac{r_\pi}{r_\pi + R_B}$$

* What if there's a diode connected?

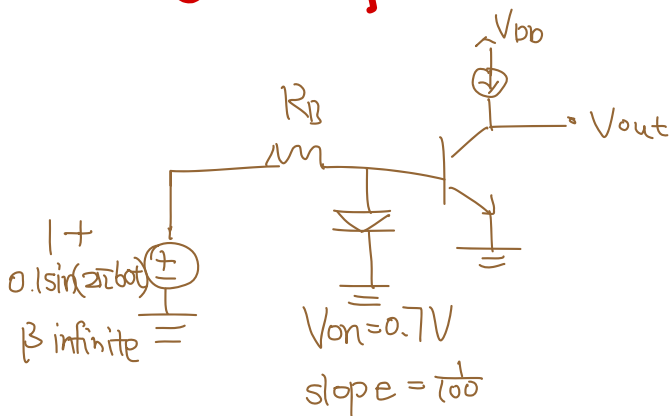

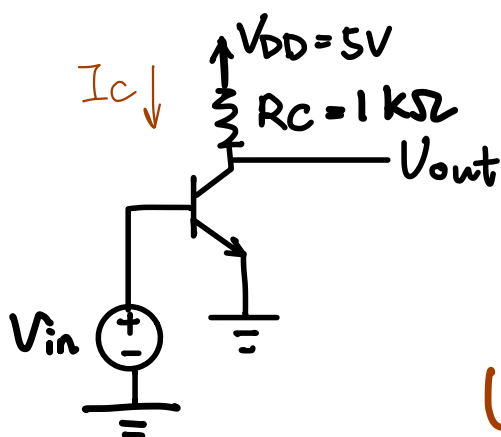A typical complete question for BJT common-emitter:



Given $V_{in} = 0.5 + 0.001 \sin(2\pi 60t)$
plot the waveform of V_{out}
(.model VAF = 100)

$$V_{out} = V_{OUT} + A_v \cdot 0.001 \sin(2\pi 60t)$$

Step 1: Find V_{OUT} (DC part of V_{out})

$$V_{OUT} = 5 - I_c \cdot (1k)$$

$$\text{Plug in } I_c = I_s \cdot (e^{q \frac{V_{BE}}{kT}} - 1) (1 + \frac{V_{CE}}{V_A})$$


$$\ast \frac{kT}{q} \approx 0.026$$

$$\Rightarrow V_{OUT} = 5 - (1 \times 10^{-18}) \times (e^{\frac{0.5}{0.026}} - 1) (1 + \frac{V_{OUT}}{100}) \cdot (1k)$$

Solve the Eq. $\Rightarrow V_{OUT} \approx 5V$

\ast Check if $V_{out} > V_{BE}$

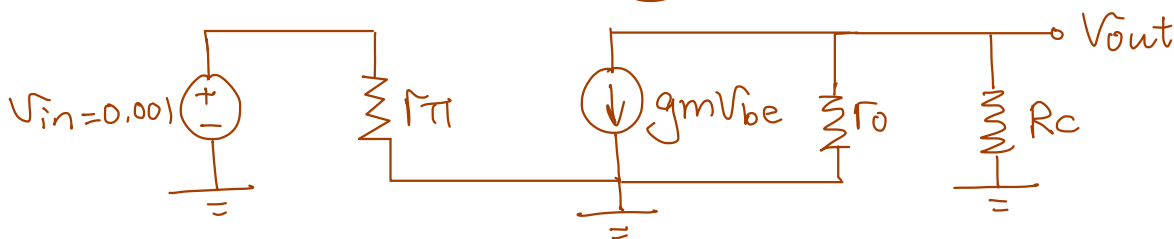Step 2: Use small-signal circuit to find A_v



$$A_v = \frac{V_{out}}{V_{in}} = -g_m (r_O \parallel R_C)$$

(If $V_A \rightarrow \infty$, no this term, $A_v = -g_m R_C$)

Step 3: find I_c , g_m , r_o , r_π if needed in A_v

$$I_c = I_s \cdot (e^{\frac{qV_{BE}}{kT}} - 1) \left(1 + \frac{V_{CE}}{V_A}\right)$$

plug in V_{out} calculated in Step 1

$$\Rightarrow I_c = 2.36 \times 10^{-10} \text{ A}$$


$$\Rightarrow g_m = \frac{I_c}{kT/q} = 9.079 \times 10^{-9}$$

$$\Rightarrow r_o = \frac{V_A}{I_c} = \frac{100}{I_c} = 4.24 \times 10^{11} \Omega$$

$$A_v = -g_m(r_o \parallel R_c) \cong -9 \times 10^{-6}$$

Step 4: Combine all to obtain V_{out}
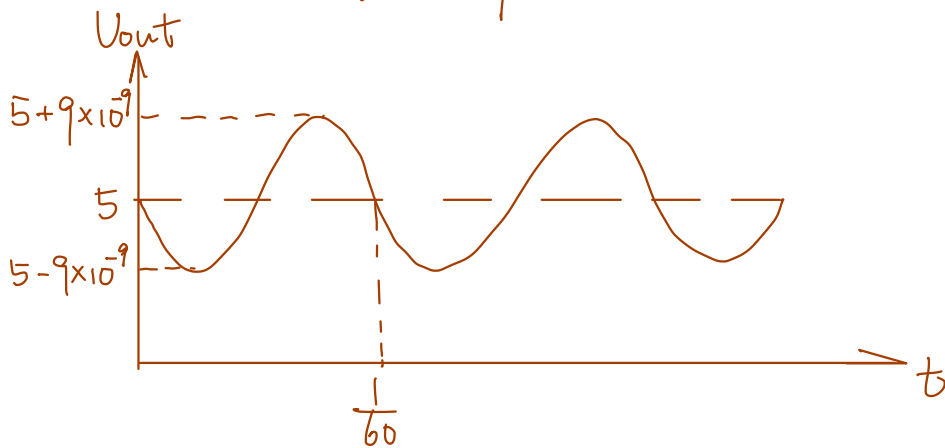
$$\begin{aligned} V_{out} &= V_{out} + A_v \cdot 0.001 \sin(2\pi 60t) \\ &= 5 - 9 \times 10^{-9} \sin(2\pi 60t) \end{aligned}$$



npn BJT Pspice Model

.model Qbreakn NPN IS=1e-18 BF=100 VAF=100

$$I_C = \textcolor{blue}{IS} \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{\textcolor{blue}{VAF}} \right)$$

$$\textcolor{blue}{BF} = \frac{I_C}{I_B} \quad I_E = I_C + I_B$$

$$g_m \cong \frac{I_C}{kT/q} \quad r_\pi = \frac{\textcolor{blue}{BF}}{g_m} \quad r_o \cong \frac{\textcolor{blue}{VAF}}{I_C}$$