
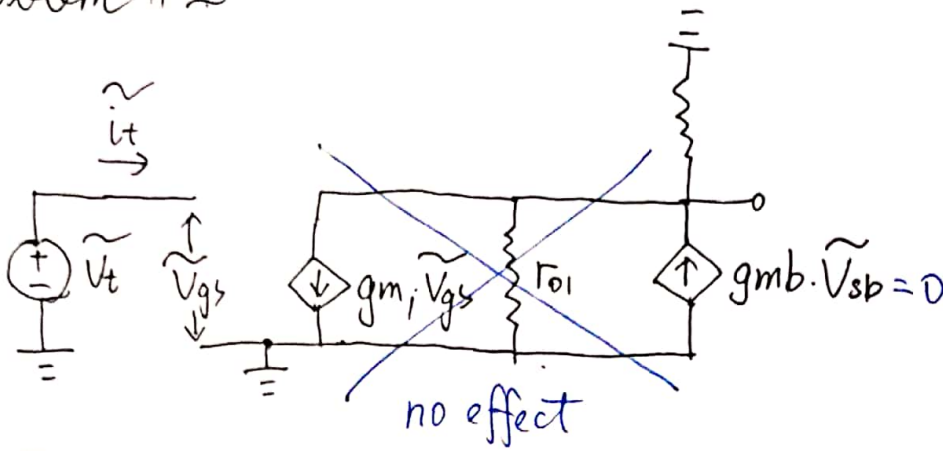


Problem #1

(1)

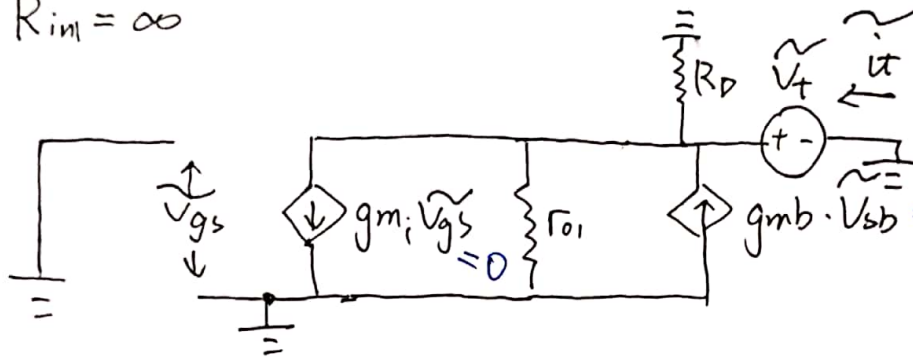

$$R_{in} = \infty$$




$$R_{out1} = \frac{V_t}{i_t} = (r_{o1} \parallel R_D)$$

(Calculate R_{in} : connect a test voltage to the input node and output node do nothing)

$R_{in} = \frac{V_t}{i_t}$ (flow into the amplifier)
(Calculate R_{out} : connect a test voltage to the output node and connect input node to ground)

$$R_{out} = \frac{V_t}{i_t} \text{ (flow into the amplifier)}$$

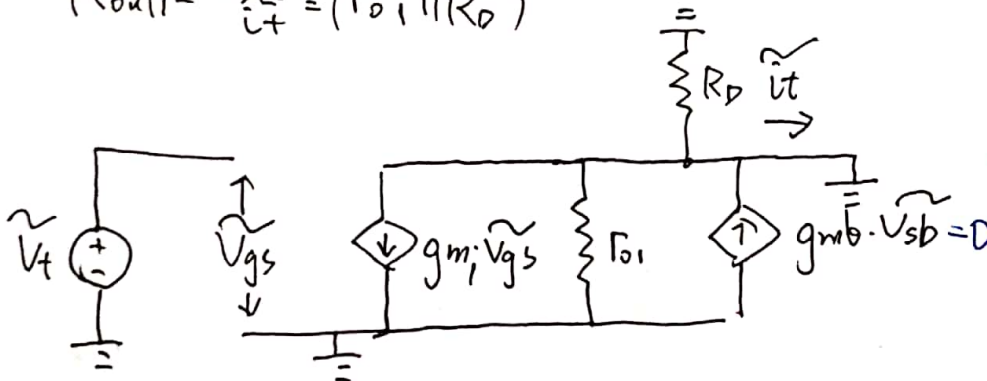(Calculate G_m : connect a test voltage to the input node and connect output node to ground)




Since r_{o1} and R_D are shorted, then $i_t = -g_{m1} \tilde{V}_{gs}$

$$G_{m1} = \frac{i_t}{V_t} = -g_{m1}$$


$$G_m = \frac{i_t}{V_t} \text{ (flow out of the amplifier)}$$

(2)

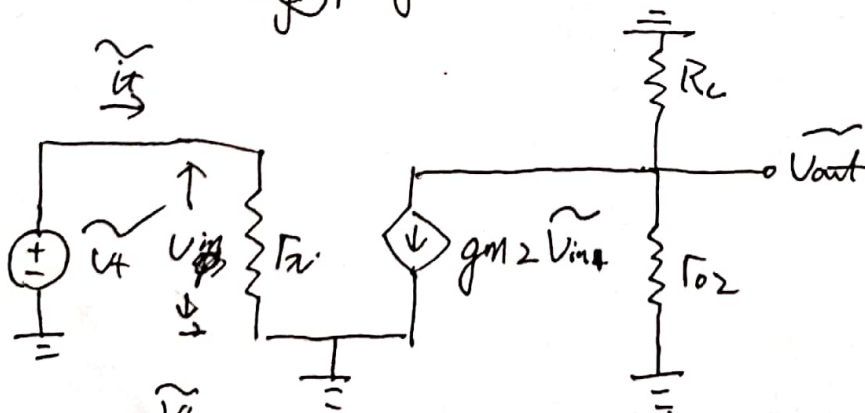

$$R_{in2} = \frac{V_t}{i_t} = r_z$$

(Reasons are the same as (1))

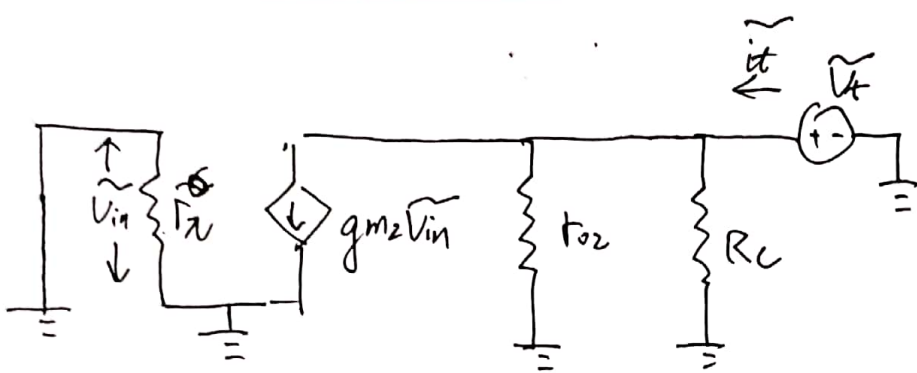


$$R_{out2} = \frac{\tilde{V}_t}{\tilde{I}_t} = (r_{o2} \parallel R_C)$$



$$\tilde{I}_t = -g_{m2} \cdot \tilde{V}_{in} \Rightarrow G_{m2} = \frac{\tilde{I}_t}{\tilde{V}_{in}} = -g_{m2}$$

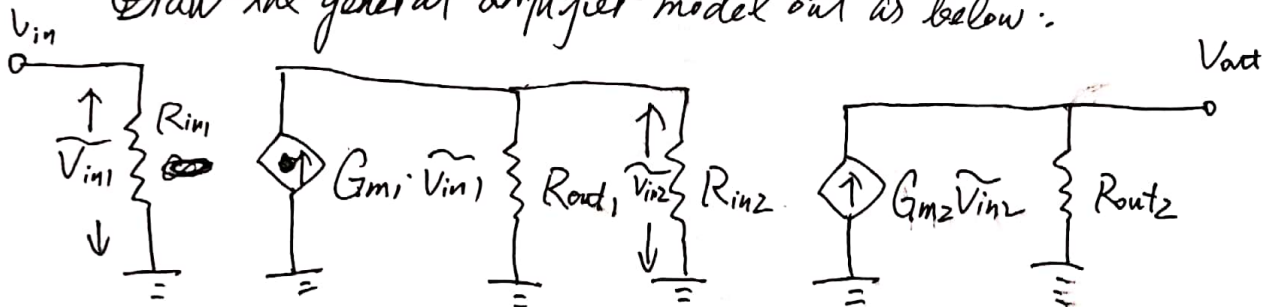(3) Draw the general amplifier model out as below:



$$\tilde{V}_{in1} = \tilde{V}_{in}$$

$$\tilde{V}_{in2} = G_{m1} \tilde{V}_{in1} \cdot (R_{out1} \parallel R_{in2}) = G_{m1} \tilde{V}_{in} (R_{out1} \parallel R_{in2})$$

$$\tilde{V}_{out} = G_{m2} \tilde{V}_{in2} R_{out2} = G_{m1} G_{m2} (R_{out1} \parallel R_{in2}) R_{out2} \tilde{V}_{in}$$


$$A_v = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = G_{m1} G_{m2} (R_{out1} \parallel R_{in2}) R_{out2}$$

$$= (-g_{m1})(-g_{m2}) [(\tau_{o1} \parallel R_D) \parallel \tau_{\pi}] (\tau_{o2} \parallel R_C)$$

$$= g_{m1} g_{m2} (\tau_{o1} \parallel R_D \parallel \tau_{\pi}) (\tau_{o2} \parallel R_C)$$

Problem # 2

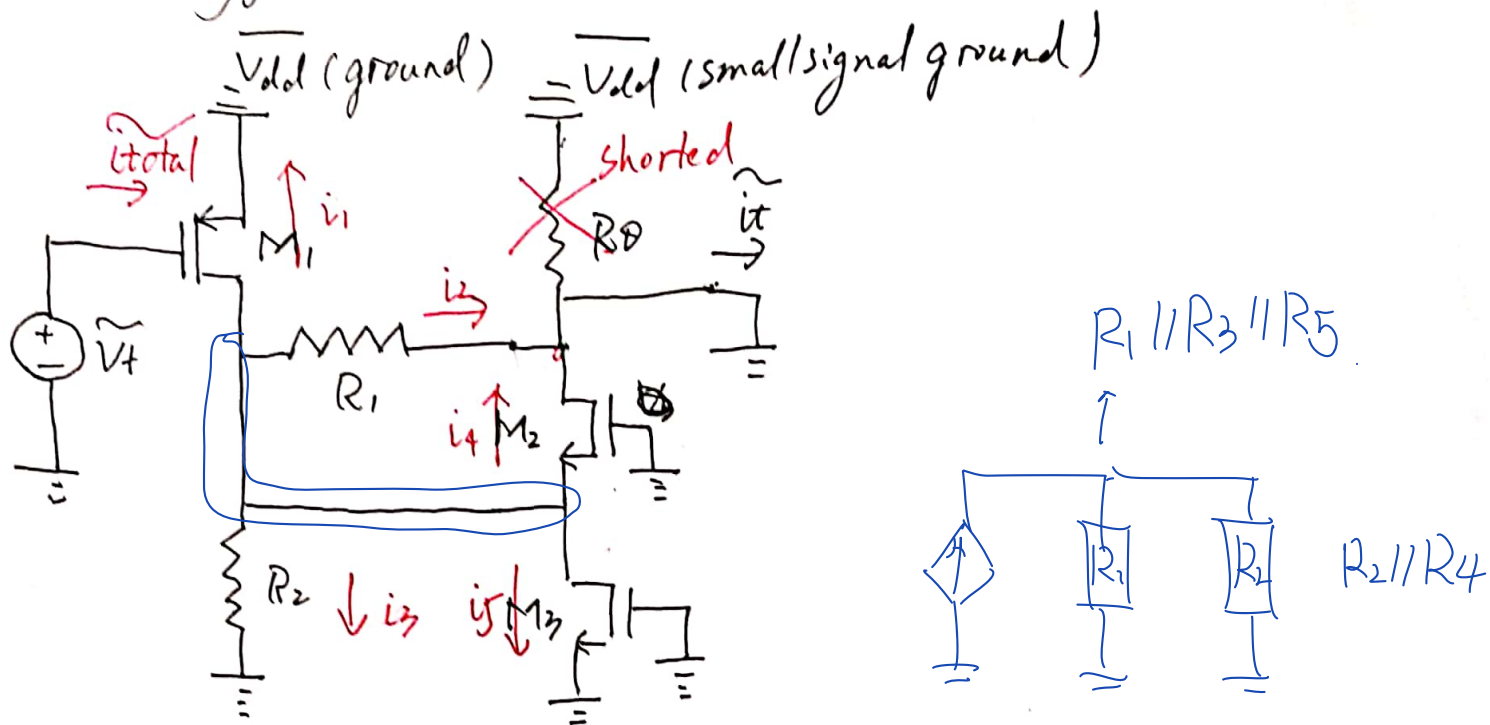(I) To identify the circuit connection, when calculating G_m , we have




R_D is shorted, M_1, R_2, R_1, M_2, M_3 are parallel connected.

Thus, $\widetilde{i_{total}} = \widetilde{i_1} + \widetilde{i_2} + \widetilde{i_3} + \widetilde{i_4} + \widetilde{i_5}$ 全是奇的。
 $\widetilde{i_t} = \widetilde{i_2} + \widetilde{i_4}$

$$\begin{aligned} \tilde{v}_t &= -g_{m1} \tilde{v}_t \times \frac{\tilde{v}_2 + \tilde{v}_4}{\tilde{v}_1 + \tilde{v}_2 + \tilde{v}_3 + \tilde{v}_4 + \tilde{v}_5} = \frac{Z_{eq}(1||3||5) \cdot (-g_{m1} v_t)}{Z_{eq}(1||3||5) + Z_{eq}(2||4)} \quad \left\{ \begin{array}{l} Z \text{ stands for} \\ \text{impedance} \end{array} \right. \\ &= \frac{-g_{m1} v_t \cdot (\Gamma_{01} || \Gamma_{02} || R_2)}{(\Gamma_{01} || \Gamma_{02} || R_2) + (R_1 || \Gamma_{02} || \frac{1}{g_{m2}} || \frac{1}{g_{mb2}})} \end{aligned}$$

$$\text{Thus, } G_m = \frac{it}{it} = -g_{m1} \frac{(r_{o1} \parallel r_{o2} \parallel R_2)}{(r_{o1} \parallel r_{o2} \parallel R_2) + (R_1 \parallel r_{o2} \parallel \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}})}$$

When calculating R_{out} , we have

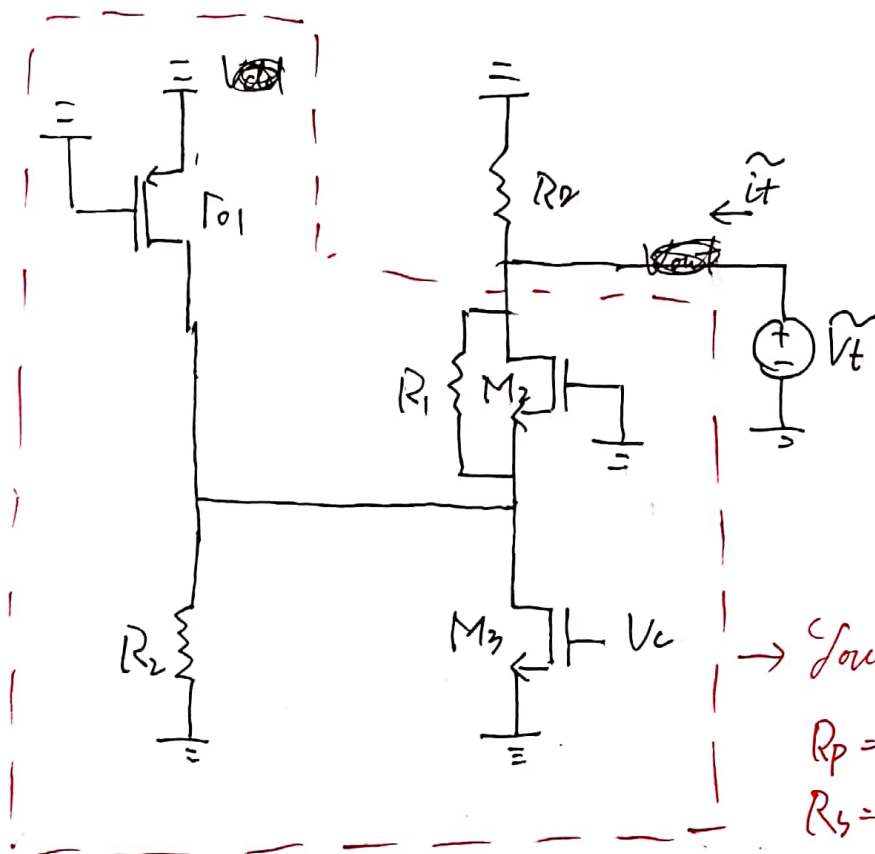

→ Source Degeneration structure $R_{out\ total}$

$$R_p = R_1 \parallel r_{o2}$$


$$R_s = r_{o3} \parallel r_{o1} \parallel R_2$$

$$R_{out} = R_0 \parallel R_{s\ total}$$

$$= R_0 \parallel [R_1 \parallel r_{o2} + r_{o3} \parallel r_{o1} \parallel R_2 + (g_{m2} + g_{mb2}) (R_1 \parallel r_{o2}) (r_{o3} \parallel r_{o1} \parallel R_2)]$$


$$A_v = G_m \cdot R_{out} = -g_{m1} \frac{(r_{o1} \parallel r_{o3} \parallel R_2)}{(r_{o1} \parallel r_{o3} \parallel R_2) + (R_1 \parallel r_{o2} \parallel \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}})} \cdot \{ R_0 \parallel [R_2 \parallel R_1 + r_{o1} \parallel r_{o3} \parallel R_2 + (g_{m2} + g_{mb2}) (R_1 \parallel r_{o2}) (r_{o3} \parallel r_{o1} \parallel R_2)] \}$$

(II)

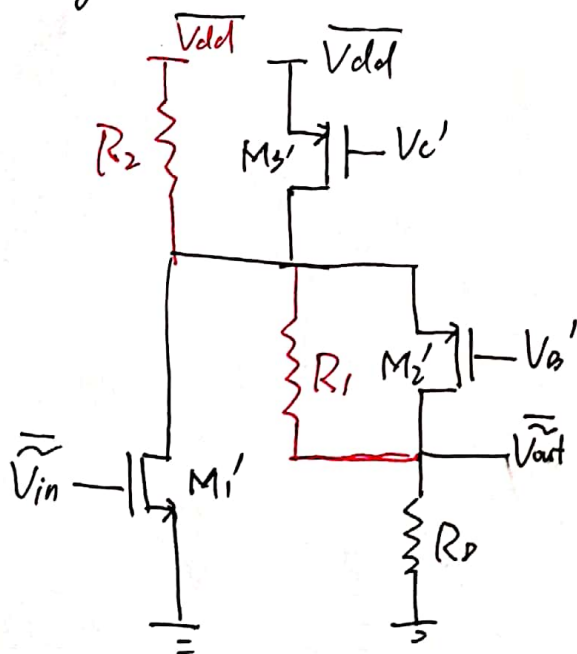

(II) The DC current source should be considered as open circuit.

For G_m :

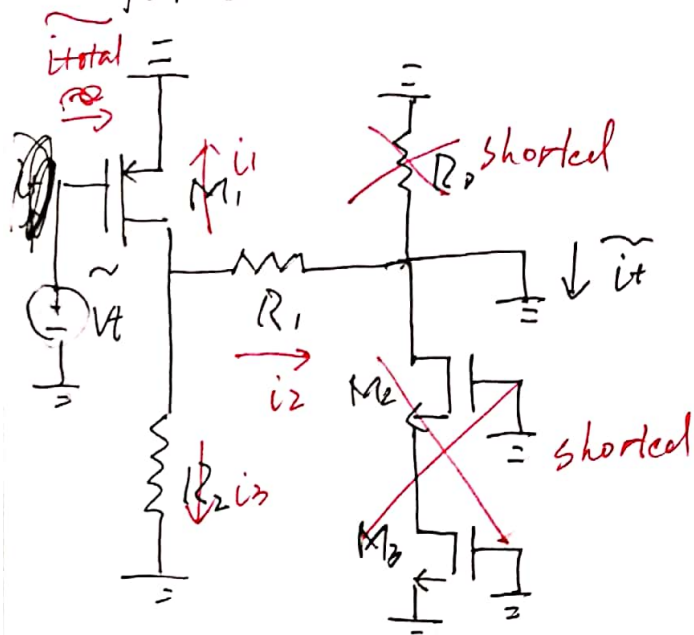

R_2, M_2, M_3 are shorted, R_1, R_2, M_1 are connected in parallel.


$$\tilde{i}_{total} = \tilde{i}_1 + \tilde{i}_2 + \tilde{i}_3 \quad \tilde{i}_t = i_2$$

$$\tilde{i}_t = -g_{m2} \tilde{v}_t \cdot \frac{\tilde{i}_2}{\tilde{i}_1 + \tilde{i}_2 + \tilde{i}_3} = -g_{m2} \tilde{v}_t \cdot \frac{Z_{eq}(1||3)}{Z_{eq}(1||3) + Z_{eq}(2)}$$

$$= -g_{m2} \tilde{v}_t \cdot \frac{r_{o1} || R_2}{r_{o1} || R_2 + R_1}$$

$$G_m = \frac{\tilde{i}_t}{\tilde{v}_t} = -g_{m2} \frac{r_{o1} || R_2}{r_{o1} || R_2 + R_1}$$


For R_{out} :

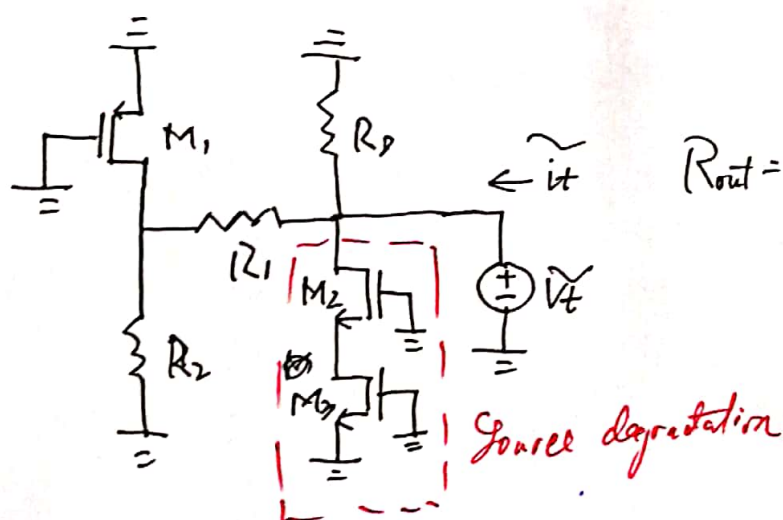

$$R_{out} = R_0 || [(R_1 + r_{o1} || R_2) || [r_{o3} + r_{o2} + (g_{m2} + g_{mb2}) r_{o2} r_{o3}]]$$


$$A_v'' = G_m R_{out}$$
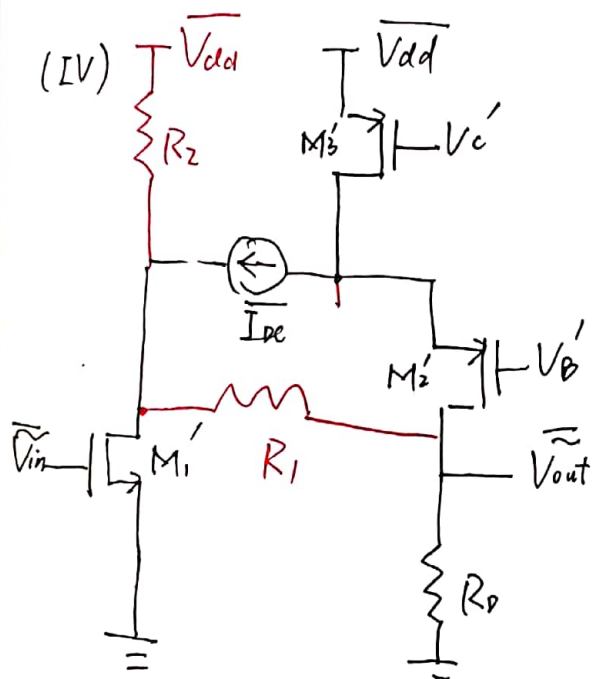
$$= -g_{m2} \frac{r_{o1} \parallel R_2}{r_{o1} \parallel R_2 + R_1} \left\{ R_2 \parallel (R_1 + r_{o1} \parallel R_2) \parallel [\Gamma_{o2} + \Gamma_{o3} + (g_{m2} + g_{mb2}) \Gamma_{o2} \Gamma_{o3}] \right\}$$



Problem # 3

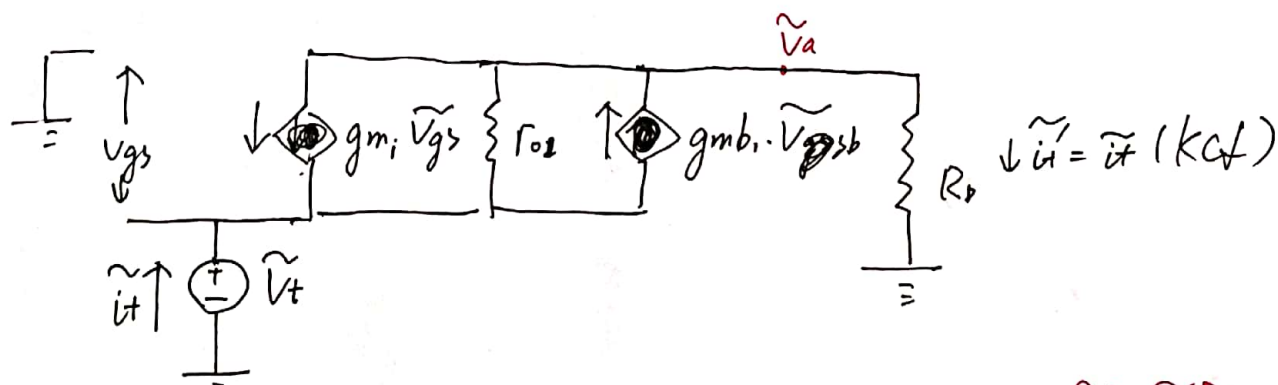(1) draw the small signal model, connect a test voltage \tilde{v}_t to the output node



$$\begin{cases} \tilde{v}_a = \tilde{i}_t \cdot R_D = \tilde{i}_t \cdot R_D \\ \tilde{i}_t = -g_{m1} \cdot \tilde{v}_{gs} + \frac{\tilde{v}_t - \tilde{v}_a}{r_{o1}} + g_{mb1} \cdot \tilde{v}_{sb} \\ \tilde{v}_{gs} = -\tilde{v}_t \\ \tilde{v}_{sb} = \tilde{v}_s - 0 = \tilde{v}_s \end{cases} \Rightarrow \begin{cases} \tilde{i}_t = g_{m1} \tilde{v}_t + \frac{\tilde{v}_t - \tilde{i}_t R_D}{r_{o1}} + g_{mb1} \tilde{v}_t \\ R_{out} = \frac{\tilde{v}_t}{\tilde{i}_t} \\ = \frac{r_{o1} + R_D}{1 + (g_{m1} + g_{mb1}) r_{o1}} \end{cases}$$

$$(2) R_D \Rightarrow \left(\frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2} \right) \leftarrow \begin{aligned} r_{o2} &\leftarrow r_{o3} \parallel r_{o4} \\ g_{m2} &\leftarrow g_{m3} + g_{m4} \\ g_{mb2} &\leftarrow g_{mb3} + g_{mb4} \end{aligned}$$

$$R_{out} = \frac{r_{o1} + \left(\frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2} \right)}{1 + (g_{m1} + g_{mb1}) \cdot r_{o1}}$$

$$(3) R_D \Rightarrow \left(\frac{1}{g_{mb3}} \parallel \frac{1}{g_{mb4}} \parallel \frac{1}{g_{m3}} \parallel \frac{1}{g_{m4}} \parallel r_{o3} \parallel r_{o4} \right)$$


$$g_{m1} + g_{mb1} \Rightarrow g_{m1} + g_{m2} + g_{mb1} + g_{mb2}$$

$$r_{o1} = r_{o1} \parallel r_{o2}$$

$$R_{out} = \frac{(r_{o1} \parallel r_{o2}) + \left(\frac{1}{g_{m3}} \parallel \frac{1}{g_{mb3}} \parallel \frac{1}{g_{m4}} \parallel \frac{1}{g_{mb4}} \parallel r_{o3} \parallel r_{o4} \right)}{1 + (g_{m1} + g_{m2} + g_{mb1} + g_{mb2}) (r_{o1} \parallel r_{o2})}$$

Problem # 4.

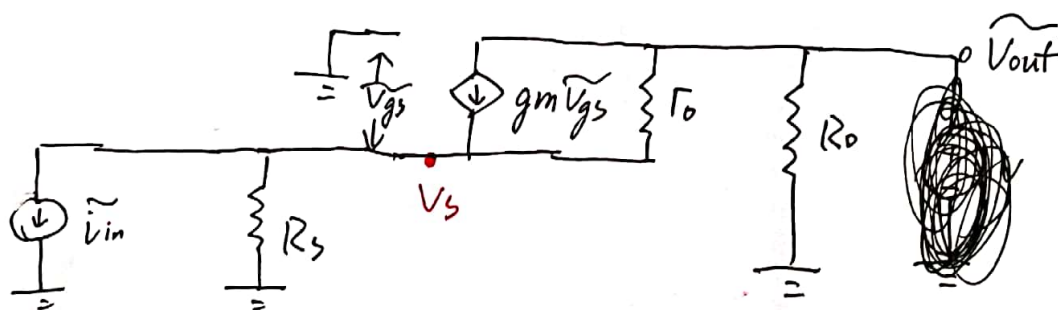(1) Draw the small signal model (since it's transimpedance, it's hard to use ~~gm~~ models solve the small signal gain).




$$\left\{ \begin{aligned} \tilde{i}_{in} + \frac{\tilde{V}_s}{R_s} &= g_m \cdot (-V_s) + \frac{\tilde{V}_{out} - \tilde{V}_s}{r_o} \quad (\text{KCL at source}) \end{aligned} \right.$$

$$\left\{ \begin{aligned} g_m \cdot (0 - \tilde{V}_s) + \frac{\tilde{V}_{out} - \tilde{V}_s}{r_o} + \frac{\tilde{V}_{out} - 0}{R_D} &= 0 \quad (\text{KCL at drain}) \end{aligned} \right.$$

$$\text{Transimpedance Gain} = \frac{\tilde{V}_{out}}{\tilde{i}_{in}}$$

$$G_{gain} = \frac{-R_D R_s (g_m r_o + 1)}{R_D + R_s + g_m r_o R_s + r_o}$$

(2)

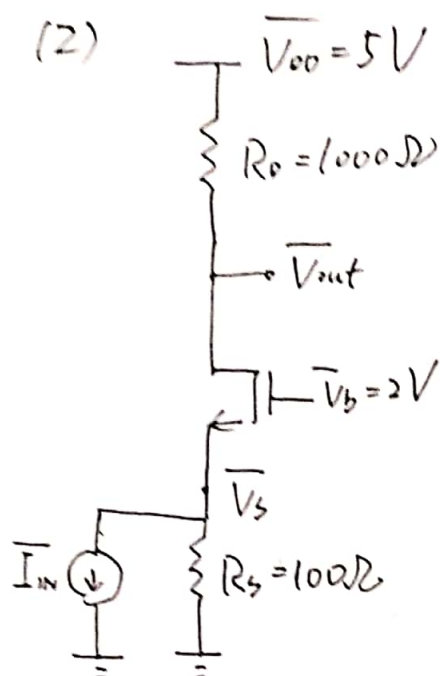

at saturation point: $\overline{V_{DS}} = \overline{V_{GS}} - \overline{V_{TH}}$

$$\overline{V_{DS}} = \overline{V_{out}} - \overline{V_S}, \overline{V_{GS}} = 2 - \overline{V_S}, \overline{V_{TH}} = 0.7 \text{ V}$$

$$\Rightarrow \overline{V_{out}} - \overline{V_S} = 2 - \overline{V_S} - 0.7 \Rightarrow \overline{V_{out}} = 1.3 \text{ V}$$

According to KCL, the current flows into the source of N-MOS is equal to the current flow out of the source,

Thus, ~~the~~ we have

$$\frac{\overline{V_S}}{R_S} + \overline{I_{IN}} = \frac{\overline{V_{DD}} - \overline{V_{out}}}{R_D} \quad (1)$$

$$\frac{\overline{V_{DD}} - \overline{V_{out}}}{R_D} = \mu C_{ox} \frac{W}{L} \cdot \frac{1}{2} (\overline{V_{GS}} - \overline{V_{TH}})^2 [1 + \lambda \overline{V_{DS}}] \quad (2)$$

$$\overline{V_{GS}} = \overline{V_{b}} - \overline{V_S} \quad (3)$$

$$\overline{V_{DS}} = \overline{V_{out}} - \overline{V_S} \quad (4)$$

$$\mu = 350 \times 10^{-4} \text{ m}^2/\text{Vs}, C_{ox} = \frac{\epsilon_0 \epsilon_r}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-12}}{9 \times 10^{-9}}$$

$$\frac{W}{L_{\text{eff}}} = \frac{W}{L_{\text{drawn}} - 2L_D} = \frac{75 \times 10^{-6}}{(2 - 0.08 \times 2) \times 10^{-6}}, \lambda = 0.1$$

$$\overline{V_{out}} = 1.3 \text{ V}, \overline{V_{DD}} = 5 \text{ V}, \overline{V_b} = 2 \text{ V}, \text{ ~~2.3 V~~}$$

In equation (2), The only unknown is

V_S , so we first solve the equation

#2

Bring all the numbers ~~and~~ and equation ①, ④ into equation ②. we have

$$\frac{5-1.3}{1000} = 350 \times 10^{-4} \times \frac{3.1 \times 8.85 \times 10^{-12}}{9 \times 10^{-9}} \times \frac{75 \times 10^{-6}}{(2-2 \times 0.08) \times 10^{-6}} \times \frac{1}{2} (2-V_s-0.7)^2 [1+0.1(1.3-V_s)]$$

$$\Rightarrow V_s = 0.14 \text{ V}$$

\Rightarrow bring $V_s = 0.14 \text{ V}$ into equation # ①. we have

$$\frac{0.14}{100} + \bar{I}_M = \frac{5-1.3}{1000} \Rightarrow \bar{I}_M = 0.0023 \text{ A}$$

Thus, the maximum \bar{I}_M for the MOSFET stays in the saturation region is 0.0023 A .

For calculating the trans-impedance, we have

$$\begin{aligned} g_m &= \frac{\partial I_{ds}}{\partial V_{gs}} = \frac{\partial \left[\mu C_{ox} \frac{W}{L_{eff}} (V_{gs} - V_{th})^2 \frac{1}{2} (1 + \lambda V_{ds}) \right]}{\partial V_{gs}} \\ &= \mu C_{ox} \frac{W}{L_{eff}} (V_{gs} - V_{th}) (1 + \lambda V_{ds}) \\ &= 350 \times 10^{-4} \times \frac{3.1 \times 8.85 \times 10^{-12}}{9 \times 10^{-9}} \times \frac{75 \times 10^{-6}}{(2-2 \times 0.08) \times 10^{-6}} \times \frac{1}{2} \times (2-0.14-0.7) \\ &\quad \times [1+0.1 \times (1.3-0.14)] \\ &= 3.52 \times 10^{-3} \text{ S} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{\partial V_{ds}}{\partial I_D} = \frac{1}{\lambda \frac{1}{2} \mu C_{ox} \frac{W}{L_{eff}} (V_{gs} - V_{th})^2} \\ &= \frac{(1 + \lambda V_{ds})}{\lambda I_D} \approx \frac{1}{\lambda I_D} = \frac{1}{\frac{5-1.3}{1000} \times 0.1} = 2703 \Omega \end{aligned}$$

$$\begin{aligned} \text{Trans-impedance}_{\text{rain}} &= \frac{-R_D R_S (g_m r_o + 1)}{R_D + R_S + g_m r_o R_S + r_o} \\ &= \frac{-(1000 \times 100 \times [3.52 \times 10^{-3} \times 2703 + 1])}{1000 + 100 + 2703 + [3.52 \times 10^{-3} \times 100 \times 2703]} = -221 \end{aligned}$$


Prob #5

(1) if $r_{o5} = \infty$, then the M_5 could be considered as an ideal DC current source. ~~Thus we have~~ Since the circuit is fully symmetric and M_5 is ideal DC, we have

$$A_{cm-cm} = 0$$

$$A_{cm-dm} = 0$$

For A_{om} : use the half-circuit method

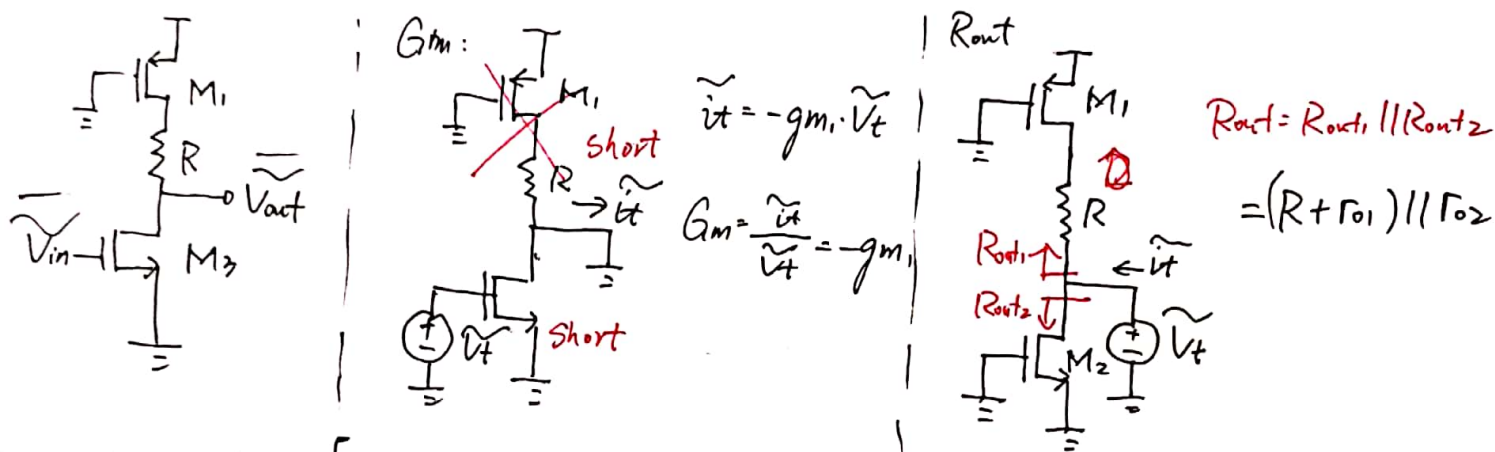

$$\text{Thus, } A_{om} = [r_{o2} \parallel (R + r_{o1})] \cdot (-g_{m1})$$

$$V_{out1} = -g_{m1} [r_{o2} \parallel (R + r_{o1})] \cdot V_{in1}$$

$$V_{out2} = -g_{m1} [r_{o2} \parallel (R + r_{o1})] \cdot V_{in2}$$


$$A_{v2} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_{m1} [r_{o2} \parallel (R + r_{o1})]$$

(2) If $r_{o5} \neq \infty$, M_5 is not an ideal DC current source.


● $A_{cm-dm} = 0$, since it's fully symmetric

$$A_{om-dm} = -g_{m1} [r_{o2} \parallel (R + r_{o1})] \text{ since it's not influenced by the current source}$$



For A_{cm} : (at the ~~back~~ next page)

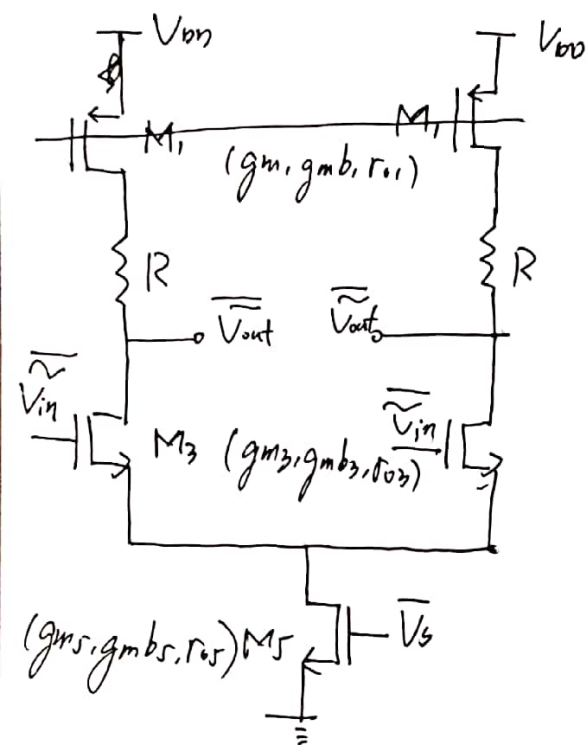

\Rightarrow

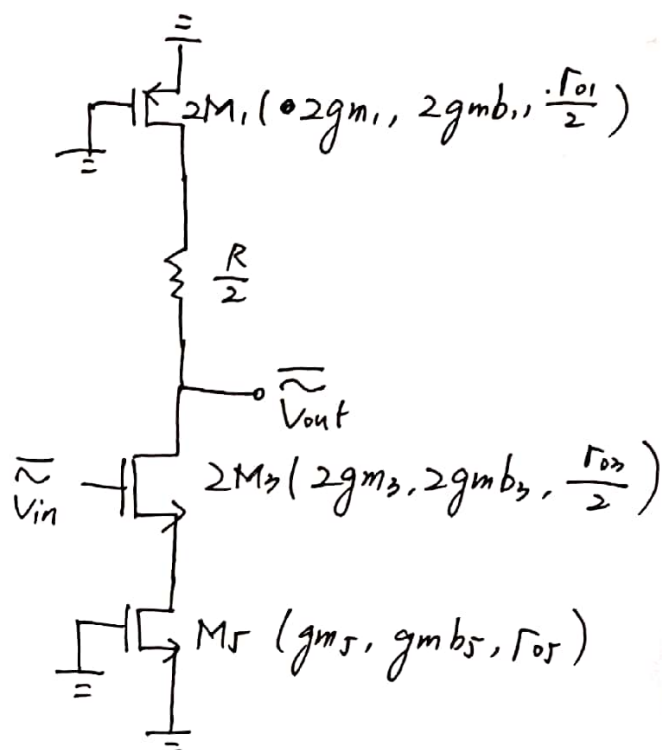

For G_m

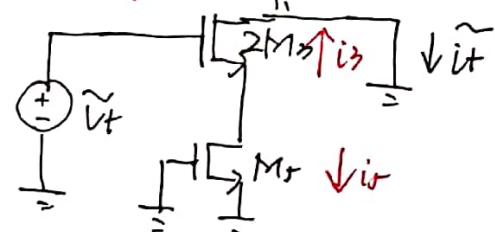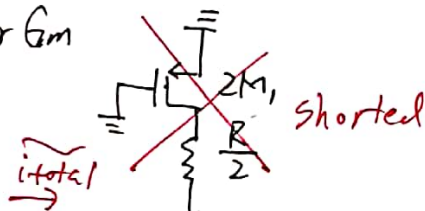

$$\tilde{i}_t = \tilde{i}_3$$

$$\tilde{i}_{total} = \tilde{i}_3 + \tilde{i}_5$$

$$\tilde{i}_t = -2g_{m3} \cdot \frac{\tilde{i}_3}{\tilde{i}_3 + \tilde{i}_5} \cdot \tilde{V}_t$$


$$= -2g_{m3} \cdot \frac{Z_{05}}{Z_T + Z_3} \cdot \tilde{V}_t$$

$$\frac{\tilde{i}_t}{\tilde{V}_t} = -2g_{m3} \cdot \frac{r_{03}/2}{r_{05} + r_{03}/2 + r_{05}r_{03}(g_{m3} + g_{mb3})}$$

$$= \frac{-2g_{m3}r_{03}}{2r_{05} + r_{03} + 2r_{05}r_{03}(g_{m3} + g_{mb3})}$$

$$A_{cm-cm} = G_m R_{out} = -2g_{m3}r_{03} \cdot \left\{ \frac{R + r_{01}}{2} \parallel \left[\frac{r_{03}}{2} + r_{05} + (g_{m3} + g_{mb3})r_{03}r_{05} \right] \right\}$$

For R_{out}

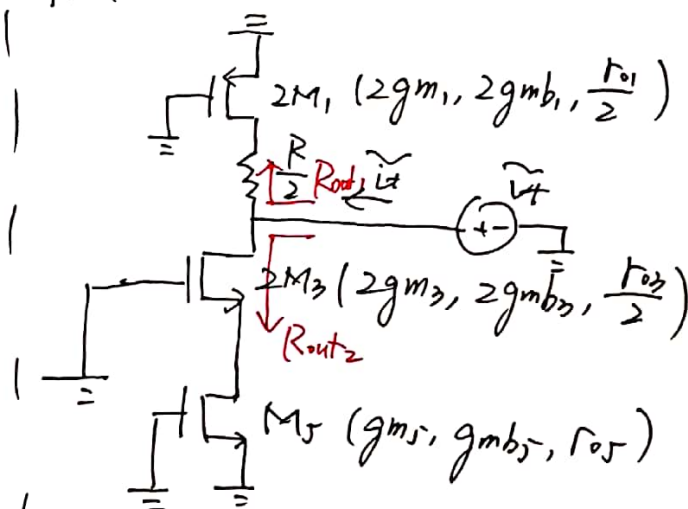

$$R_{out} = R_{out1} \parallel R_{out2}$$

$$= \left(\frac{R}{2} + \frac{r_{01}}{2} \right) \parallel \left[\frac{r_{03}}{2} + r_{05} + (2g_{m3} + 2g_{mb3}) \frac{r_{03}}{2} r_{05} \right]$$

$$= \frac{R + r_{01}}{2} \parallel \left[\frac{r_{03}}{2} + r_{05} + (g_{m3} + g_{mb3})r_{03}r_{05} \right]$$